

Consider a resistive-load inverter circuit with $V_{DD} = 5V$, $k_n' = 20 \mu A/V^2$, $V_{TO} = 0.8V$, $R_L = 200k\Omega$, and $W/L = 2$. Calculate the critical voltages (V_{OL} , V_{OH} , V_{IL} , V_{IH}) on the V_{TC} and find the noise margins of the circuit.

⇒ When the i/p voltage is low i.e. when the driver n-MOS transistor is cut-off, the o/p high voltage can be found as,

$$V_{OH} = V_{DD} = 5V$$

In Resistive load inverter, the transconductance of the driver transistor is $k_n = k_n' (W/L) = 40 \mu A/V^2$ and hence,

$$k_n R_L = 8 V^{-1}$$

The output low voltage V_{OL} is calculated by

$$V_{OL} = V_{DD} - V_{TO} + \frac{1}{k_n R_L} - \sqrt{\left(V_{DD} - V_{TO} + \frac{1}{k_n R_L}\right)^2 - \frac{2V_{DD}}{k_n R_L}}$$

$$= 5 - 0.8 + \frac{1}{8} - \sqrt{\left(5 - 0.8 + \frac{1}{8}\right)^2 - \frac{2 \cdot 5}{8}}$$

$$V_{OL} = 0.147V$$

The critical voltage V_{IL} is given by

$$V_{IL} = V_{TO} + \frac{1}{k_n R_L} = 0.8 + \frac{1}{8} = 0.925V$$

Finally, the critical voltage V_{IH} is given by,

$$V_{IH} = V_{TO} + \sqrt{\frac{8}{3} \frac{V_{DD}}{k_n R_L}} - \frac{1}{k_n R_L} = 0.8 + \sqrt{\frac{8}{3} \cdot \frac{5}{8}} - \frac{1}{8} = 1.97V$$

$$\text{Low noise margin } NML = V_{IL} - V_{OL} = 0.93 - 0.15 = 0.78V$$

$$\text{High noise margin } NMH = V_{OH} - V_{IH} = 5.0 - 1.97 = 3.03V$$

Consider the following inverter design problem:
 $V_{DD} = 5V$, $k_n' = 30 \mu A/V^2$ and $V_{T0} = 1V$, design a resistive-load inverter circuit with $V_{OL} = 0.2V$. Specifically, determine the (W/L) ratio of the driver transistor and the value of the load resistor R_L that achieve the required V_{OL} is $34k\Omega$.

\Rightarrow The driver transistor is operating in the linear region when the output voltage is equal to V_{OL} , and the i/p voltage is equal to $V_{OH} = V_{DD}$

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{k_n'}{2} (W/L) \cdot [2 \cdot (V_{OH} - V_{T0}) \cdot V_{OL} - V_{OL}^2]$$

Assuming $V_{OL} = 0.2V$ & using the given values for the power supply voltage, the driver threshold voltage and the driver transconductance k_n' , we obtain the following equation,

$$\therefore \frac{5 - 0.20}{R_L} = \frac{30 \times 10^{-6}}{2} \cdot \frac{W}{L} [(2 \times 4 \times 0.20) - (0.20)^2]$$

$$\therefore \frac{W}{L} \cdot R_L = 2.05 \times 10^5 \Omega$$

$$\boxed{\therefore \frac{W}{L} = 6}$$