 


Static Timing Analysis

>>> Short Notes
>>> Concept
>>> Numericals


• HARSHIT GUPTA



Introduction

- Effective methodology for verifying the timing characteristics of a design without the use of test vectors
- Conventional verification techniques are inadequate for complex designs
 - Simulation time using conventional simulators
 - Thousands of test vectors are required to test all timing paths using logic simulation
 - Increasing design complexity & smaller process technologies
 - Increases the number of iterations for STA


Simulation vs. Static timing

 

STA approach typically takes a fraction of the time it takes to run logic simulation on a large design and guarantees 100% coverage of all true timing paths in the design without having to generate test vectors

OVERVIEW

Previous Verification Flow

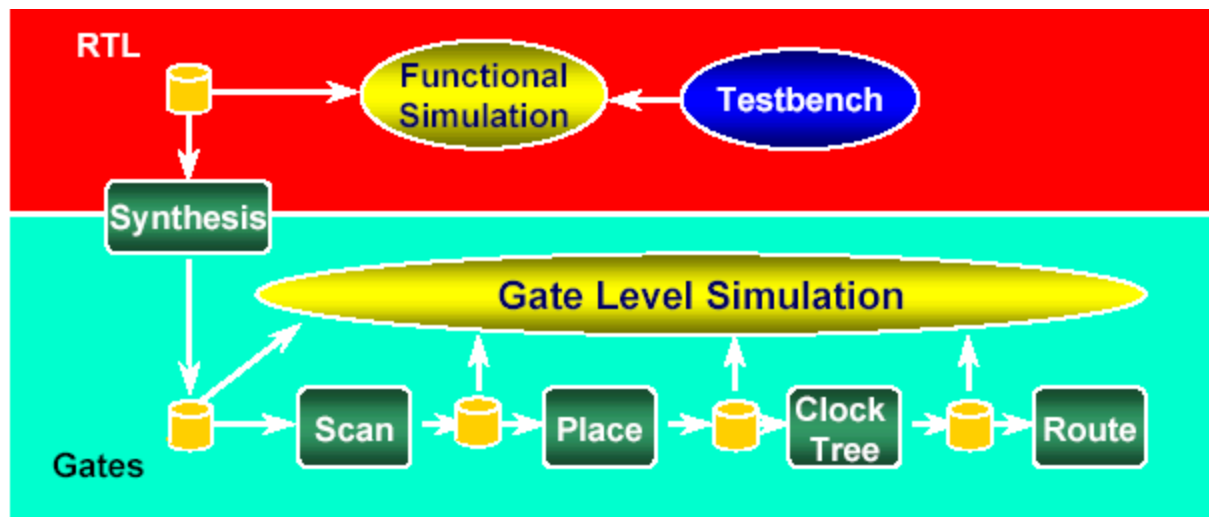

OVERVIEW


- Requires extensive vector creation
- Valid for FPGAs and smaller ASICs
- Falls apart on multi-million gate ASICs

What is Static Timing Analysis?


Static Timing Analysis is a method for determining if a circuit meets timing constraints without having to simulate

- Much faster than timing-driven, gate-level simulation
- Proper circuit functionality is not checked
- Vector generation NOT required

STA in ASIC Design Flow – Pre layout

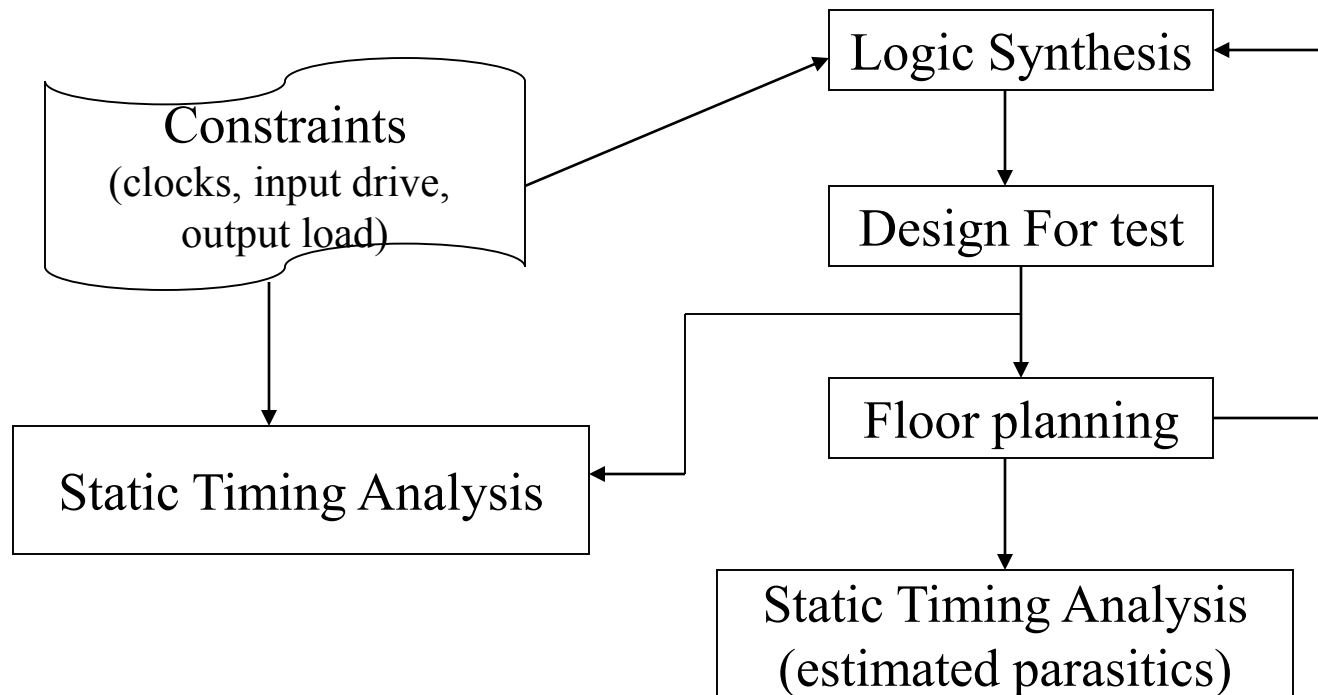

STA in ASIC Design Flow – Post Layout

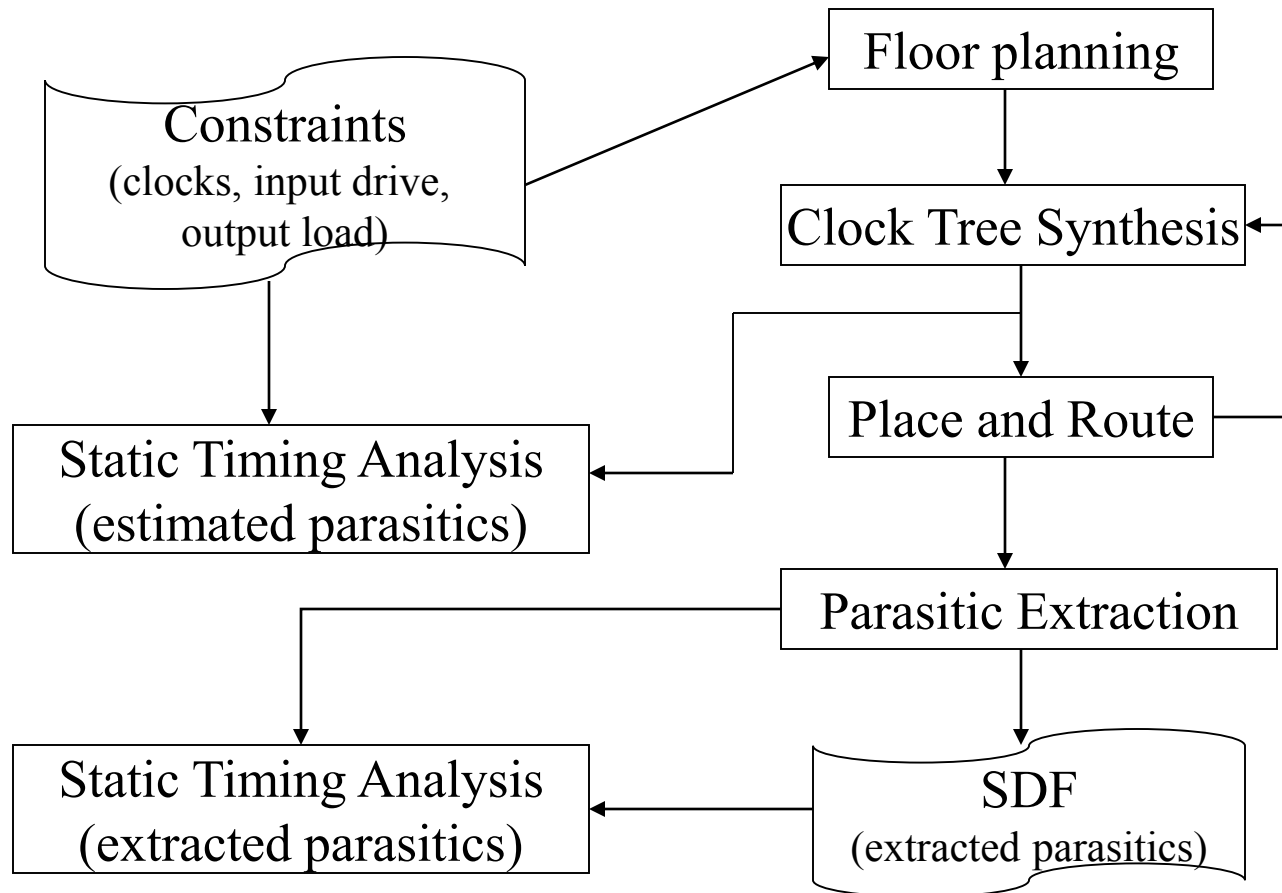

2 Types of Timing Verification

Dynamic Timing Simulation

Advantages

- Can be *very* accurate (spice-level)

Disadvantages

- Analysis quality depends on stimulus vectors
- Non-exhaustive, slow

Examples:

VCS, Spice, ACE

2 Types of Timing Verification

Static Timing Analysis (STA)


Advantages

- Fast, exhaustive
- Better analysis checks against timing requirements

Disadvantage


- Less accurate
- Must define timing requirements/exceptions
- Difficulty handling asynchronous designs, false paths

Three Steps in Static Timing Analysis

 

- Circuit is broken down into sets of timing paths
- Delay of each path is calculated
- Path delays are checked to see if timing constraints have been met

What is a Timing Path?

 

A Timing Path is a point-to-point path in a design which can propagate data from one flip-flop to another

❖ Each path has a **start point** and an **endpoint**


➤ **Start point:**

➤ Input ports Clock pins of flip-flops

➤ **Endpoints:**

➤ Output ports Data input pins of flip-flops

Organizing Timing Paths Into Groups

 


Timing paths are grouped into path groups by the clocks controlling their endpoints

Synthesis tools like PrimeTime and Design Compiler organize timing reports by path groups

Net and Cell Timing Arcs

 
The actual path delay is the sum of net and cell delays along the timing path




Net and Cell Delay

“Net Delay” refers to the total time needed to charge or discharge all of the parasitics of a given net

 - Total net parasitics are affected by
 - net length
 - net fanout
- Net delay and parasitics are typically
 - Back-Annotated (Post-Layout) from data obtained from an extraction tool
 - Estimated (Pre-Layout)



Cell Delay

 

In ASICs, the delay of a cell is affected by:

- The input transition time (or slew rate)
- The total load “seen” by the output transistors


Net capacitance and “downstream” pin capacitances

- These will affect how quickly the input and output transistors can “switch”
- Inherent transistor delays and “internal” net delays

Clocked Storage Elements


Transparent Latch, Level Sensitive

 - data passes through when clock high, latched when clock low





D-Type Register or Flip-Flop, Edge-Triggered

 - data captured on rising edge of clock, held for rest of cycle



Flip-Flops

 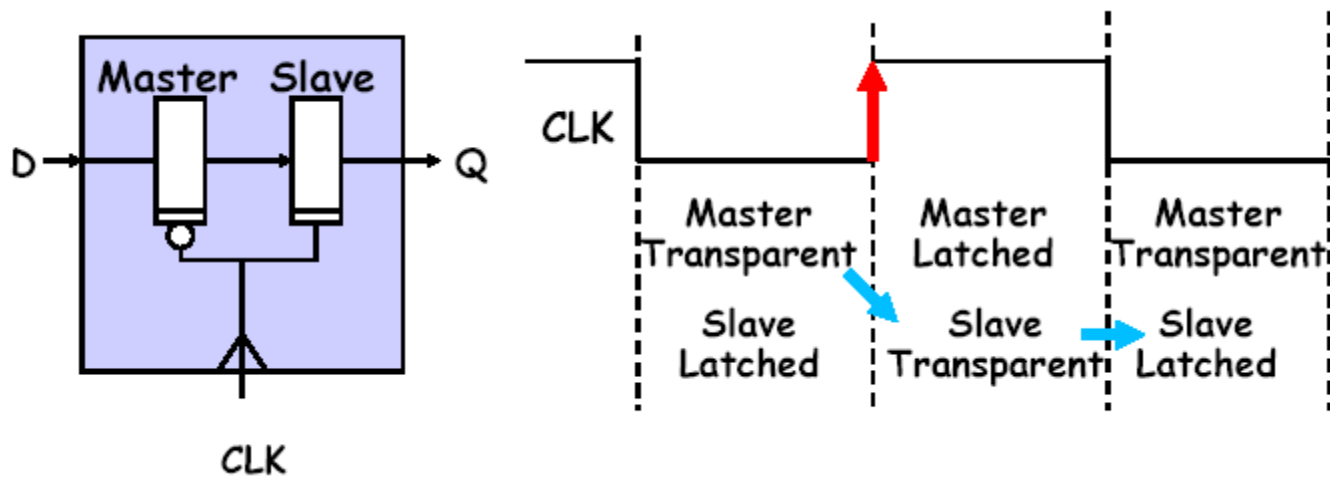

Basic terminologies


- Pulse Width
- Setup & Hold times
- Signal slew
- Clock latency
- Clock Skew
- Input arrival time
- Output required time
- Slack and Critical path
- Recovery & Removal times
- False paths
- Multi-cycle paths

Pulse Width

- Pulse width
 - It is the time between the active and inactive states of the same signal

Setup and Hold time

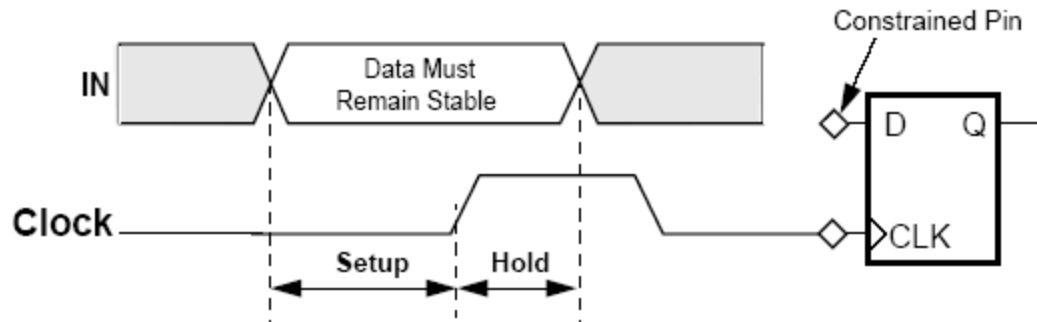
- Setup time
 - For an edge triggered sequential element, the setup time is the time interval before the active clock edge during which the data should remain unchanged
- Hold time
 - Time interval after the active clock edge during which the data should remain unchanged



Both the above 2 timing violations can occur in a design when
clock path delay > data path delay


Signal Slew

 - Signal (Clock/Data) slew
 - Amount of time it takes for a signal transition to occur
 - Accounts for uncertainty in Rise and fall times of the signal
 - Slew rate is measured in volts/sec



Clock Latency

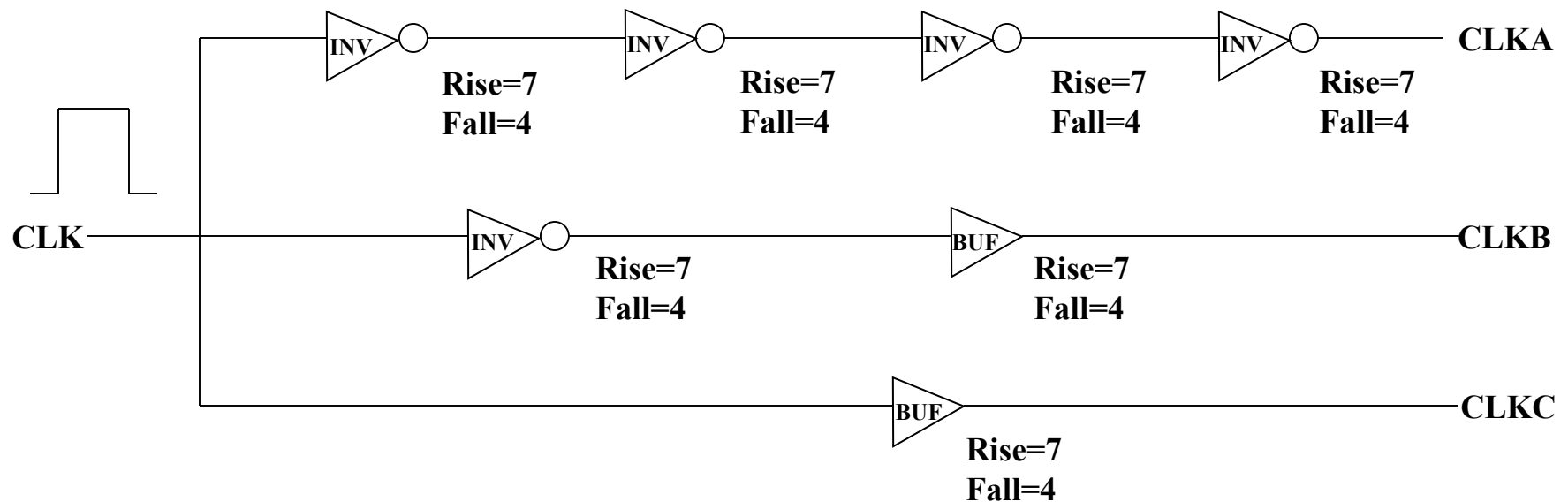- Clock Latency
 - Difference between the reference (source) clock slew to the clock tree endpoint signal slew values
 - Rise latency and fall latency are specified



Clock Latency

CLK to CLKA	Min Latency Rise = 4 + 7 + 4 + 7 = 22 (maximum value) Min Latency Fall = 7 + 4 + 7 + 4 = 22
CLK to CLKB	Min Latency Rise = 4 + 4 = 8 Min Latency Fall = 7 + 7 = 14
CLK to CLKC	Min Latency Rise = 7 Min Latency Fall = 4 (minimum value)

$$\text{Average} = (22 + 22 + 8 + 14 + 7 + 4) / 6 = 12.83$$

$$\text{Standard Deviation} = \sqrt{\left[\left(22^2 + 22^2 + 8^2 + 14^2 + 7^2 + 4^2 \right) / 6 \right] - (12.83)^2} = 7.13$$

Therefore:

Minimum Latency			
Minimum	Maximum	Average	Std. Dev.
4	22	12.83	7.13


Clock Skew

- Clock Skew is a measure of the difference in latency between any two leaf pins in a clock tree.
 - between CLKA and CLKB
 - rise = $22 - 8 = 14$
 - fall = $22 - 14 = 8$
 - between CLKB and CLKC
 - rise = $8 - 7 = 1$
 - fall = $14 - 4 = 10$
 - between CLKA and CLKC
 - rise = $22 - 7 = 15$
 - fall = $22 - 4 = 18$

It is also defined as the difference in time that a single clock signal takes to reach two different registers


Input Arrival time

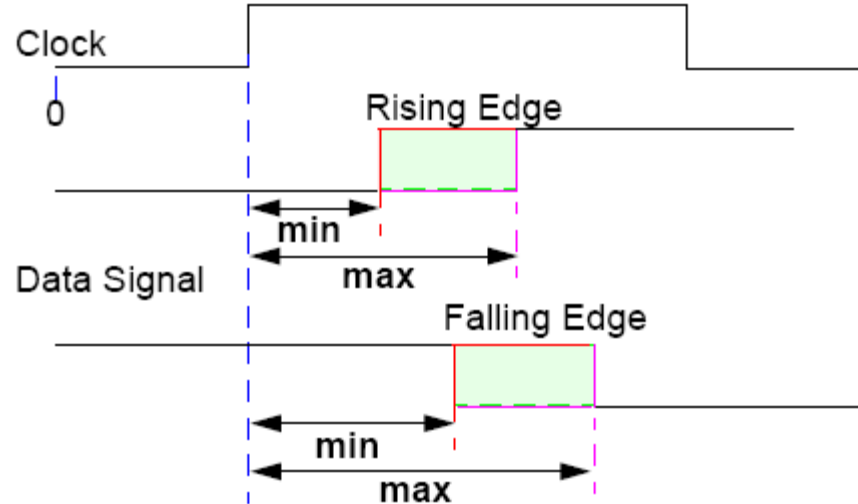- Input Arrival time
 - An arrival time defines the time interval during which a data signal can arrive at an input pin in relation to the nearest edge of the clock signal that triggers the data transition



Output required time

 - Output required time
 - Specifies the data required time on output ports.



Slack and Critical path


➤ Slack

- It is the difference between the required (constraint) time and the arrival time (inputs and delays).
- Negative slack indicates that constraints have not been met, while positive slack indicates that constraints have been met.
- Slack analysis is used to identify timing critical paths in a design by the static timing analysis tool

➤ Critical path

- Any logical path in the design that violates the timing constraints
- Path with a negative slack

Slack Analysis – Data Path types

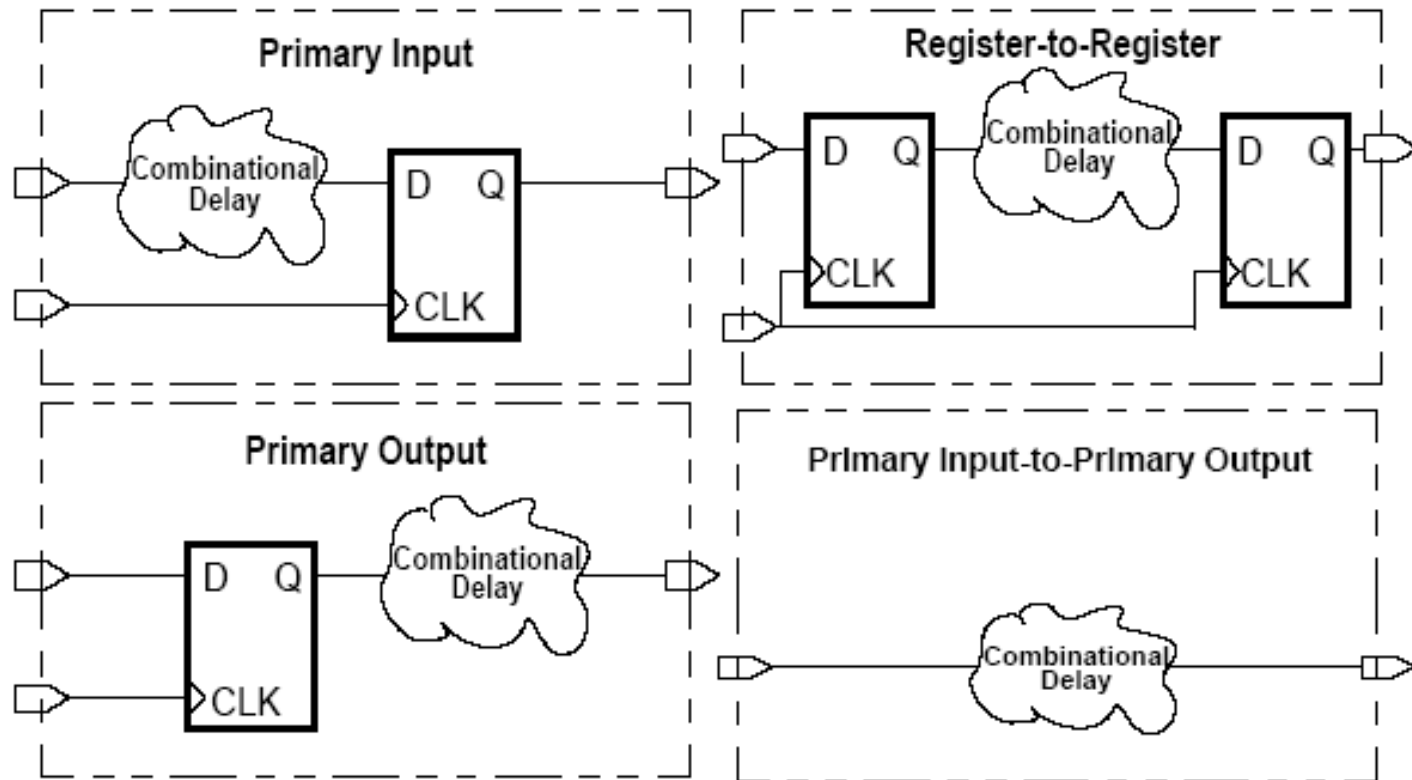

Slack analysis – data path types

- Primary input-to-register paths
 - Delays off-chip + Combinational logic delays up to the first sequential device.
- Register-to-primary output paths
 - Start at a sequential device
 - CLK-to-Q transition delay + the combinational logic delay + external delay requirements
- Register-to-register paths
 - Delay and timing constraint (Setup and Hold) times between sequential devices for synchronous clocks + source and destination clock propagation times.
- Primary input-to-primary output paths
 - Delays off-chip + combinational logic delays + external delay requirements.

Hold Slack calculation

- Actual data arrival time definition

Data Input Arrival Timemin + Data path delaymin

If the data path starts in a primary input,

Data Input arrivalmin = Input arrival timemin

If the data path starts at a register,

(Source Clock Edgemin + Source Clock Path Delaymin) =
Data Input Arrivalmin


- Required Stability time definition

(Destination Clock Edgemax + Destination Clock Path Delaymax) +
Hold = Required Stability Timemax

- Hold Slack definition

Actual Data Arrivalmin - Required Stability Timemax

Calculate the hold slack

 

Source Clock signal timing parameters:

Min Edge = 8.002 ns

Min clock path delay = 0.002 ns

Min Data path delay = 0.802 ns


Hold time constraint = 1.046 ns

Destination Clock signal timing parameters:

Max Edge = 2.020 ns

Max clock path delay = 0.500 ns

Hold slack calculation

 

Source Clock signal timing parameters:

Min Edge = 8.002 ns

Min clock path delay = 0.002 ns


Min Data path delay = 0.802 ns

Hold time constraint = 1.046 ns

Destination Clock signal timing parameters:

Max Edge = 2.020 ns

Max clock path delay = 0.500 ns

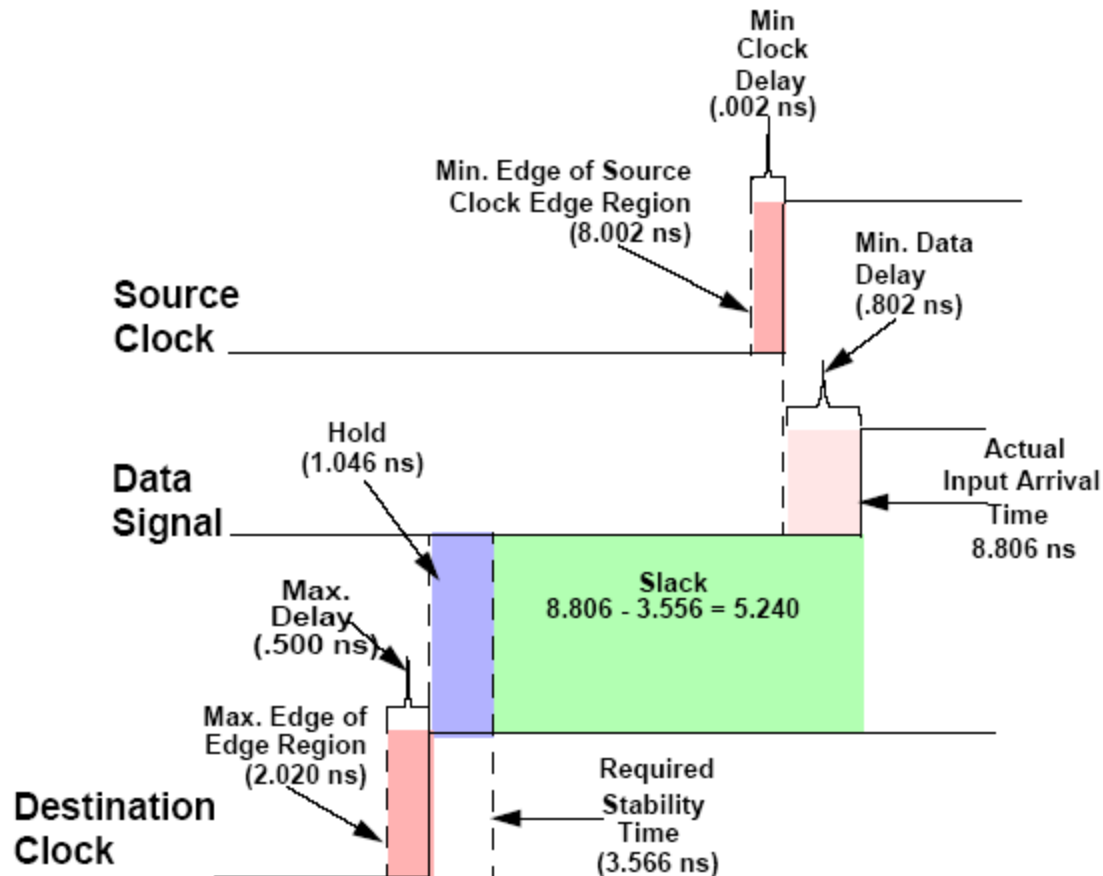

Setup Slack calculation

- Actual data arrival time definition

$\text{Data Input Arrival Time}_{\max} + \text{Data path delay}_{\max}$

If the data path starts in a primary input,

$\text{Data Input arrival}_{\max} = \text{Input arrival time}_{\max}$

If the data path starts at a register,

$(\text{Source Clock Edge}_{\max} + \text{Source Clock Path Delay}_{\max}) =$
 $\text{Data Input Arrival}_{\max}$


- Required Stability time definition

$(\text{Destination Clock Edge}_{\min} + \text{Destination Clock Path Delay}_{\min}) -$
 $\text{Setup} = \text{Required Stability Time}_{\min}$

- Setup slack definition

$\text{Required Stability Time}_{\min} - \text{Actual Data Arrival}_{\max}$

Calculate the setup slack

 

Source Clock signal timing parameters:

Max Edge = 2.002 ns

Max clock path delay = 0.002 ns

Min Data path delay = 13.002 ns


Setup time constraint = 0.046 ns

Destination Clock signal timing parameters:

Min Edge = 20.02 ns

Min clock path delay = 0.500 ns

Setup slack calculation

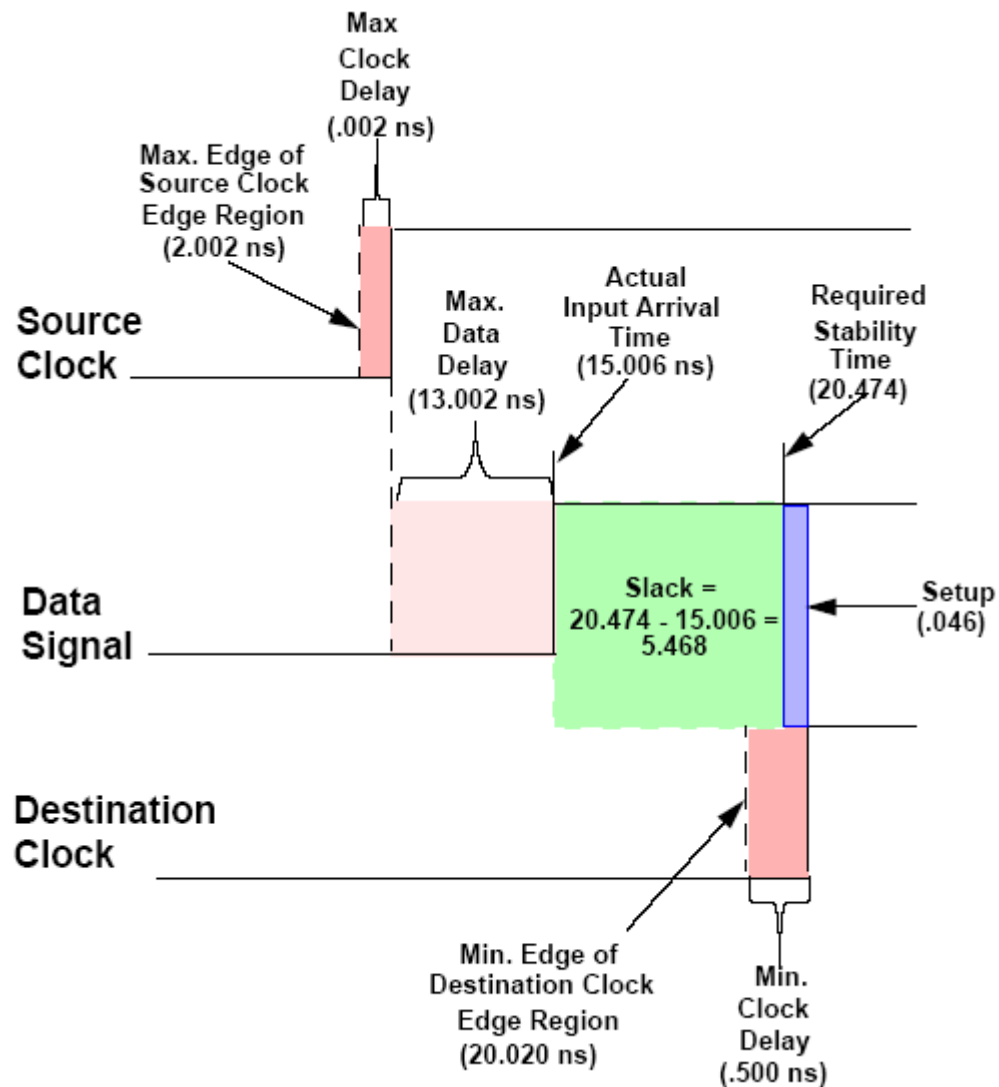


Recovery and Removal time

- Recovery time
 - Like setup time for asynchronous port (set, reset)
- Removal time
 - Like hold time for asynchronous port (set, reset)

- Recovery time
 - It is the time available between the asynchronous signal going inactive to the active clock edge
- Removal time
 - It is the time between active clock edge and asynchronous signal going inactive


False Paths

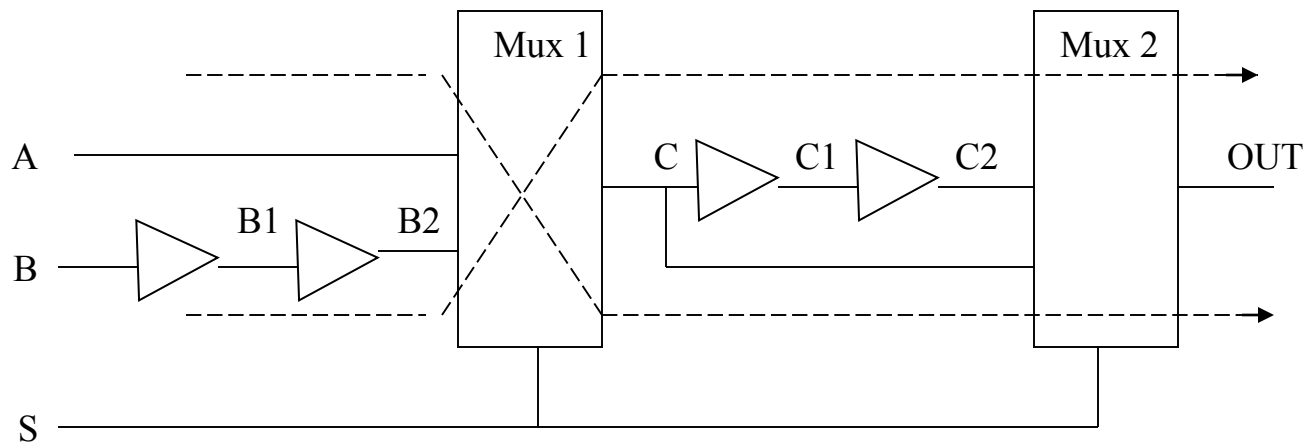- False paths
 - Paths that physically exist in a design but are not logic/functional paths
 - These paths never get sensitized under any input conditions



Multi-cycle paths

 - Multi-cycle paths
 - Data Paths that require more than one clock period for execution



Sequential Circuit Timing

Objectives


This section covers several timing considerations encountered in the design of synchronous sequential circuits. It has the following objectives:

- Define the following global timing parameters and show how they can be derived from the basic timing parameters of flip-flops and gates.
 - Maximum Clock Frequency
 - Maximum allowable clock skew
 - Global Setup and Hold Times
- Discuss ways to control the loading of data into registers and show why gating the clock signal to do this is a poor design practice.

Maximum Clock Frequency

- The clock frequency for a synchronous sequential circuit is limited by the timing parameters of its flip-flops and gates. This limit is called *the maximum clock frequency* for the circuit. The *minimum clock period* is the reciprocal of this frequency.
- Relevant timing parameters
 - ❖ Gates:
 - Propagation delays: $\min t_{PLH}$, $\min t_{PHL}$, $\max t_{PLH}$, $\max t_{PHL}$
 - ❖ Flip-Flops:
 - Propagation delays: $\min t_{PLH}$, $\min t_{PHL}$, $\max t_{PLH}$, $\max t_{PHL}$
 - Setup time: t_{su}
 - Hold time: t_h

➤ Example

 


$$T_W \geq \max t_{PFF} + t_{su}$$

For the 7474, $\max t_{PLH} = 25\text{ns}$, $\max t_{PHL} = 40\text{ns}$, $t_{su} = 20\text{ns}$

$$T_W \geq \max (\max t_{PLH} + t_{su}, \max t_{PHL} + t_{su})$$



$$T_W \geq \max (25+20, 40+20) = 60$$

➤ Example

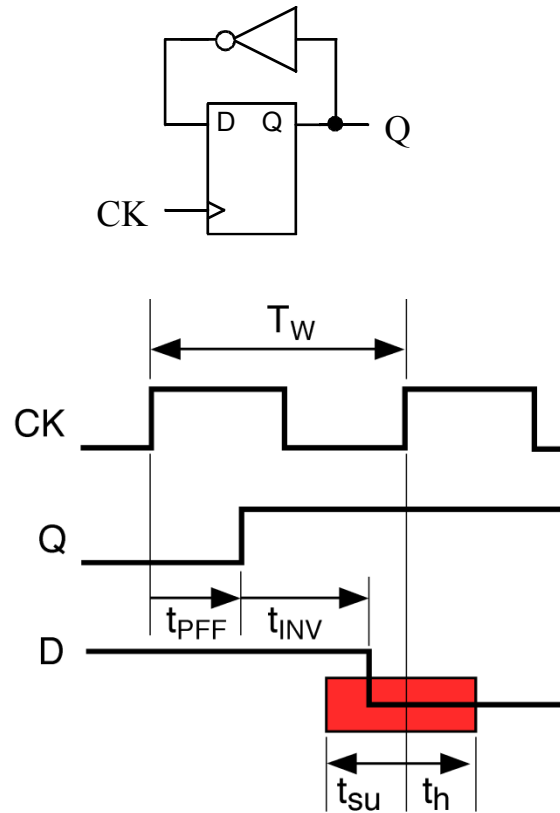


$$T_W \geq \max t_{PFF} + \max t_{PINV} + t_{su}$$

➤ Example

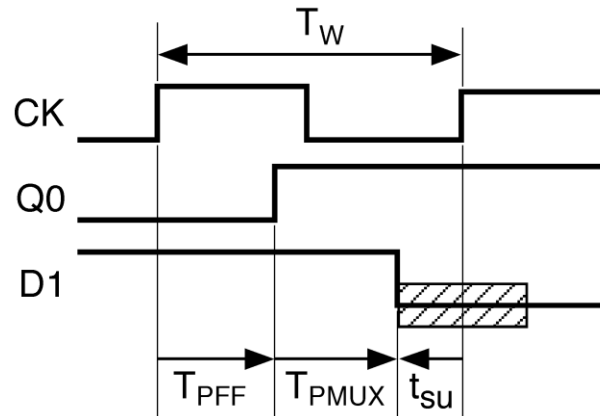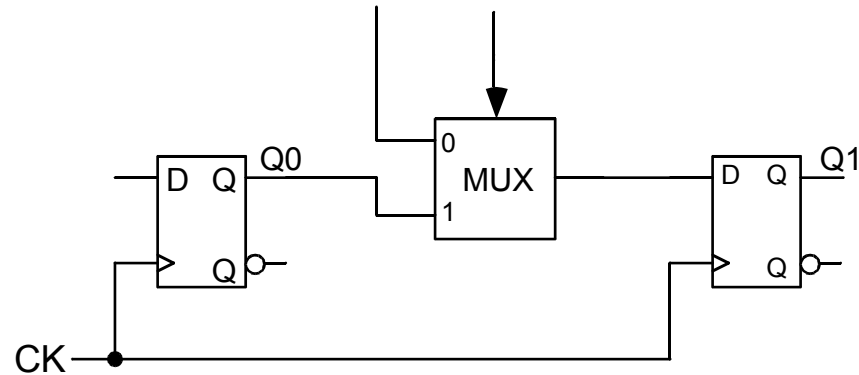

$$T_W \geq \max t_{PFF} + \max t_{PMUX} + t_{su}$$

➤ Example

 

	t_p	t_{su}
D Flip-Flop:	20 ns	5 ns
JK Flip-Flop:	25 ns	10 ns
AND Gate:	12 ns	
OR Gate:	10 ns	

Paths from Q1 to Q1: None

Paths from Q1 to Q2: $T_W \geq \max t_{PDFF} + t_{JKsu} = 20 + 10 = 30 \text{ ns}$

$T_W \geq \max t_{PDFF} + \max t_{AND} + t_{JKsu} = 20 + 12 + 10 = 42 \text{ ns}$

Paths from Q2 to Q1: $T_W \geq \max t_{PJKFF} + t_{OR} + T_{Dsu} = 25 + 10 + 5 = 40 \text{ ns}$





Paths from Q2 to Q2: $T_W \geq \max t_{PJKFF} + \max t_{AND} + t_{JKsu} = 25 + 12 + 10 = 47 \text{ ns}$

$TW \geq 47 \text{ ns}$

Clock Skew

- If a clock edge does not arrive at different flip-flops at exactly the same time, then the clock is said to be *skewed* between these flip-flops. The difference between the times of arrival at the flip-flops is said to be the amount of *clock skew*.
- Clock skew is due to different delays on different paths from the clock generator to the various flip-flops.
 - Different length wires (wires have delay)
 - Gates (buffers) on the paths
 - Flip-Flops that clock on different edges (need to invert clock for some flip-flops)
 - Gating the clock to control loading of registers (a very bad idea)

    - Example (Effect of clock skew on clock rate)
 - Clock C2 skewed after C1





$$T_W \geq \max T_{PFF} + \max t_{OR} + t_{su}$$

(if clock not skewed, i.e., $t_{INV} = 0$)

$$T_W \geq \max T_{PFF} + \max t_{OR} + t_{su} - \min t_{INV}$$

(if clock skewed, i.e., $t_{INV} > 0$)

➤ Clock C1 skewed after C2

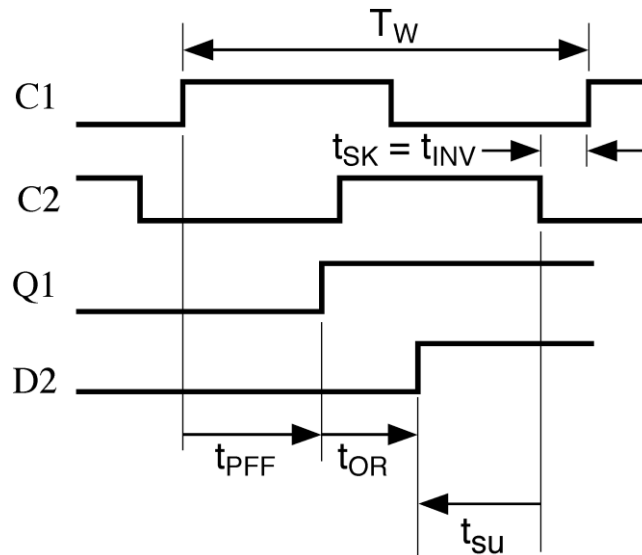 



$$T_W \geq \max T_{PFF} + \max t_{OR} + t_{su}$$

(if clock not skewed, i.e., $t_{INV} = 0$)

$$T_W \geq \max T_{PFF} + \max t_{OR} + t_{su} + \max t_{INV}$$

(if clock skewed, i.e., $t_{INV} > 0$)

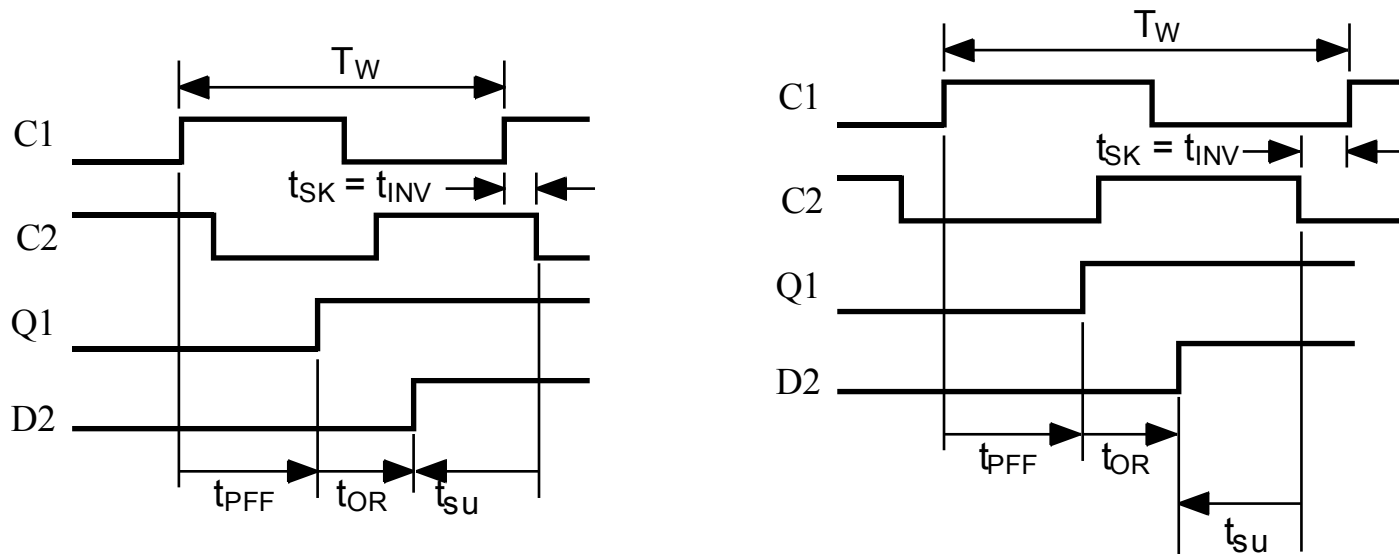 ➤ Summary of maximum clock frequency calculations




C2 skewed after C1: $T_w \geq \max T_{PFF} + \max t_{NET} + t_{su} - \min t_{INV}$


C2 skewed before C1: $T_w \geq \max T_{PFF} + \max t_{NET} + t_{su} + \max t_{INV}$

Maximum Allowable Clock Skew

 - How much skew between C1 and C2 can be tolerated in the following circuit?





- Case 1: C2 delayed after C1

 



$$t_{PFF} > t_h + t_{SK}$$

$$t_{SK} < \min t_{PFF} - t_h$$

➤ Case 2: C1 delayed from C2

  

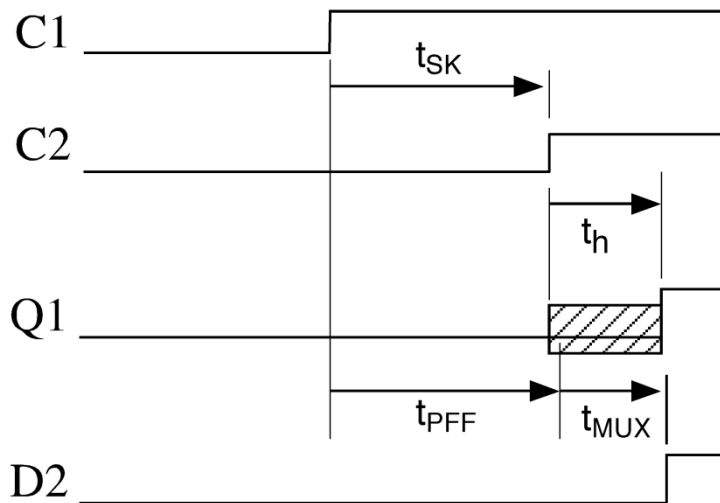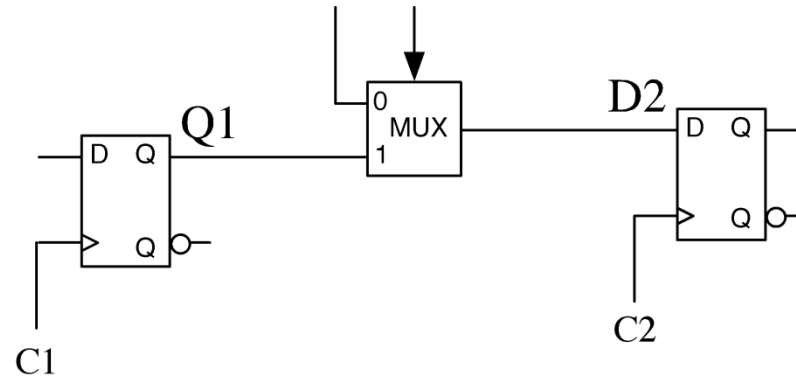
- How does additional delay between the flip-flops affect the skew calculations?



$$t_{sk} \leq \min t_{PFF} - t_h$$


$$t_{sk} \leq \min t_{PFF} + \min t_{MUX} - t_h$$

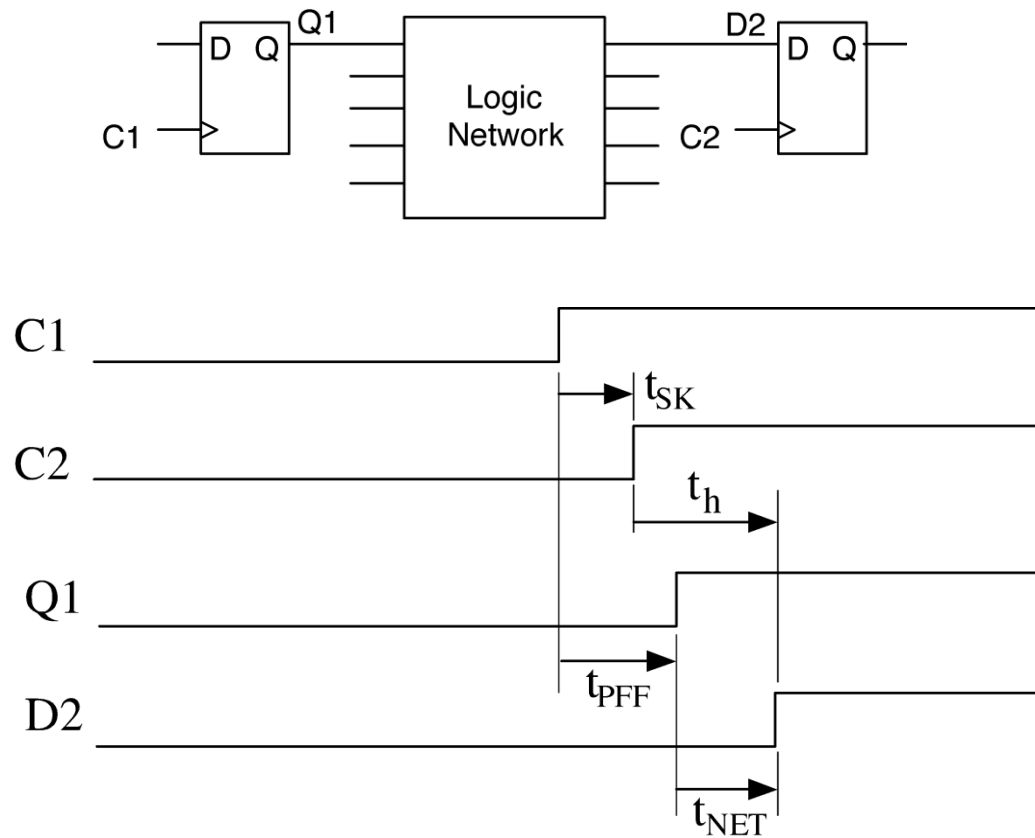
➤ Summary of allowable clock skew calculations



$$t_{SK} + t_h \leq t_{PFF} + t_{NET}$$
$$t_{SK} \leq \min t_{PFF} + \min t_{NET} - t_h$$

 - Example: What is the minimum clock period for the following circuit under the assumption that the clock C2 is skewed after C1 (i.e., C2 is delayed from C1)?



 

- First calculate the maximum allowable clock skew.

$$t_{SK} < \min t_{PFF} + \min t_{N1} - t_h$$

- Next calculate the minimum clock period due to the path from Q1 to D2.

$$T_W > \max t_{PFF} + \max t_{N1} + t_{su} - \min t_{SK}$$

- Finally calculate the minimum clock period due to the path from Q2 to D1


$$T_W > \max t_{PFF} + \max t_{N1} + t_{su} + \max t_{SK}$$

$$T_W > \max t_{PFF} + \max t_{N2} + t_{su} + (\min t_{PFF} + \min t_{N1} - t_h)$$



$$T_W > \max t_{PFF} + \min t_{PFF} + \max t_{N2} + \min t_{N1} + t_{su} - t_h$$

Global Setup Time, Hold Time and Propagation Delay

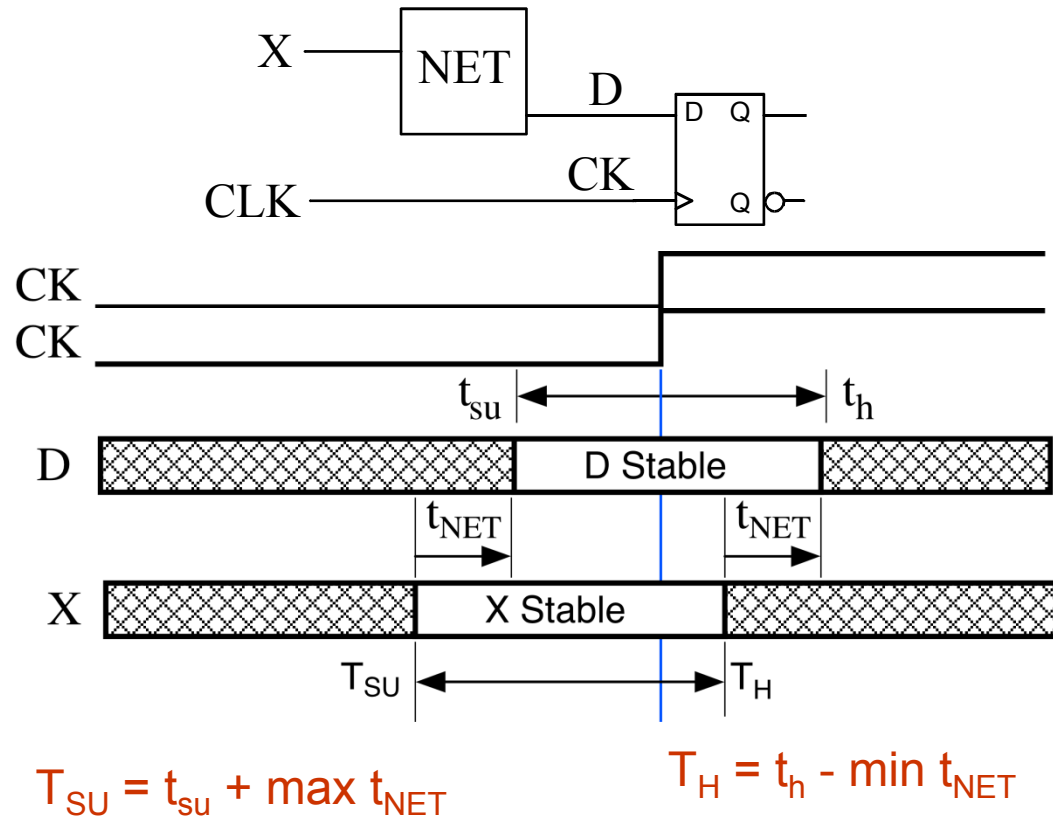- Global setup and hold times (data delayed)



  
➤ Global setup & hold time (clock delayed)



$$T_{SU} = t_{su} - \min t_C$$



$$T_H = t_h + \max t_C$$

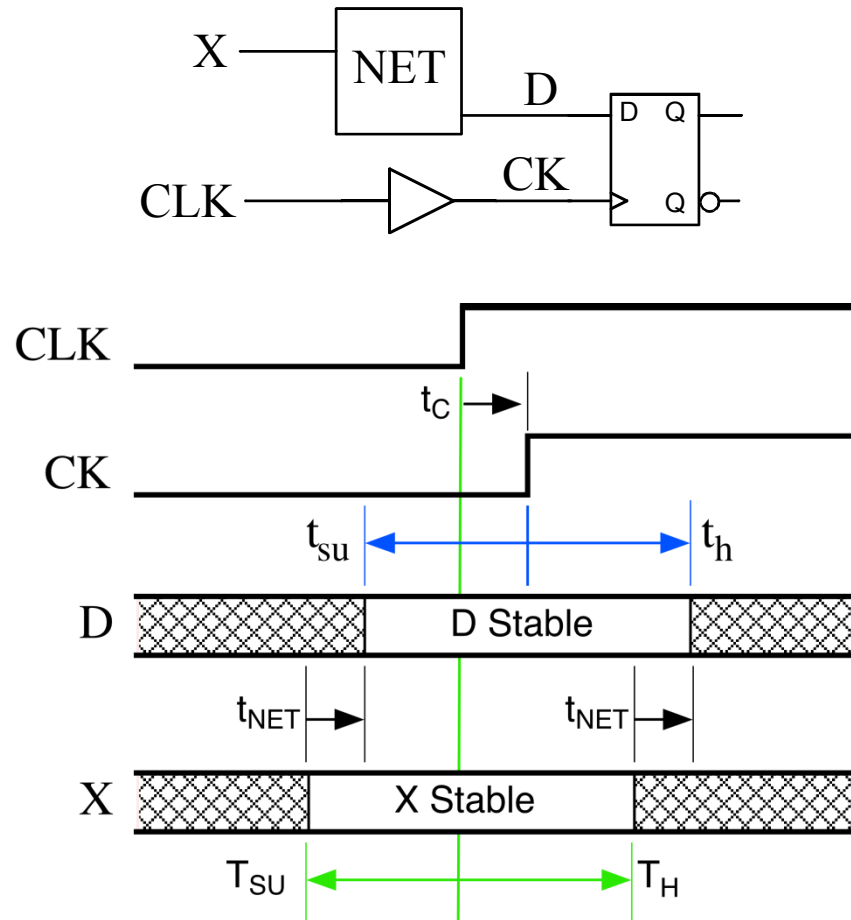➤ Global setup & hold time (data & clock delayed)





$$T_{SU} = t_{su} + \max(t_{NET}) + \max(t_c) \quad T_H = t_h - \min(t_{NET}) + \max(t_c)$$

➤ Global propagation delay

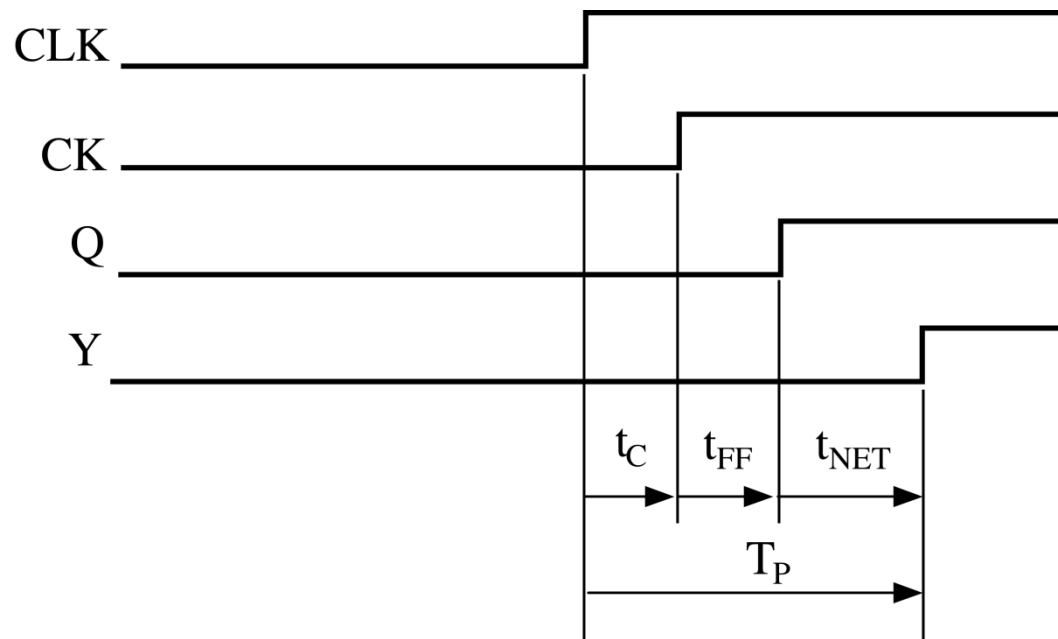 

$$T_P = t_C + t_{FF} + t_{NET}$$

➤ Summary of global timing parameters

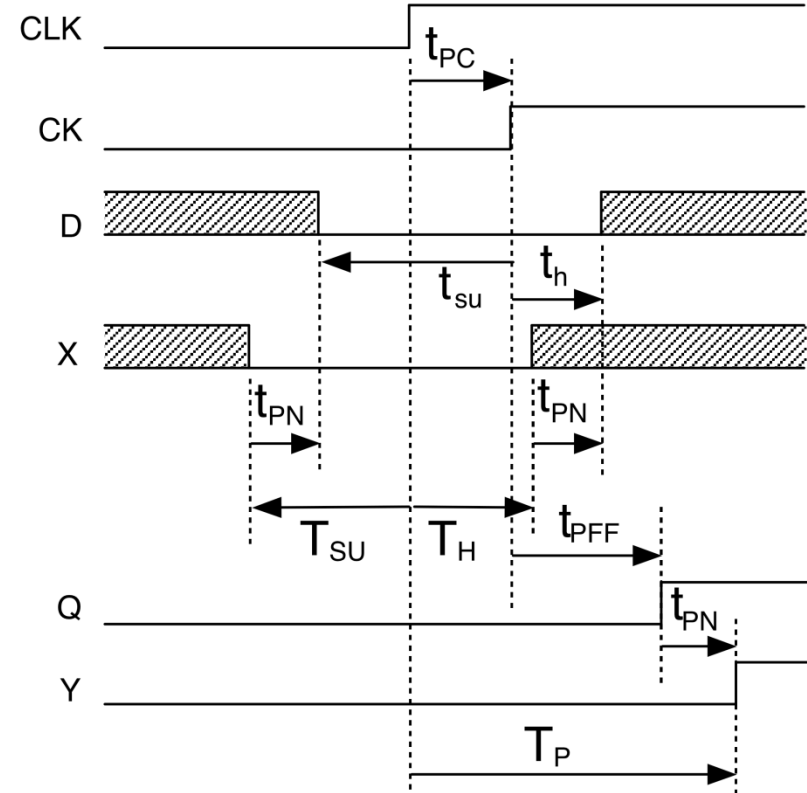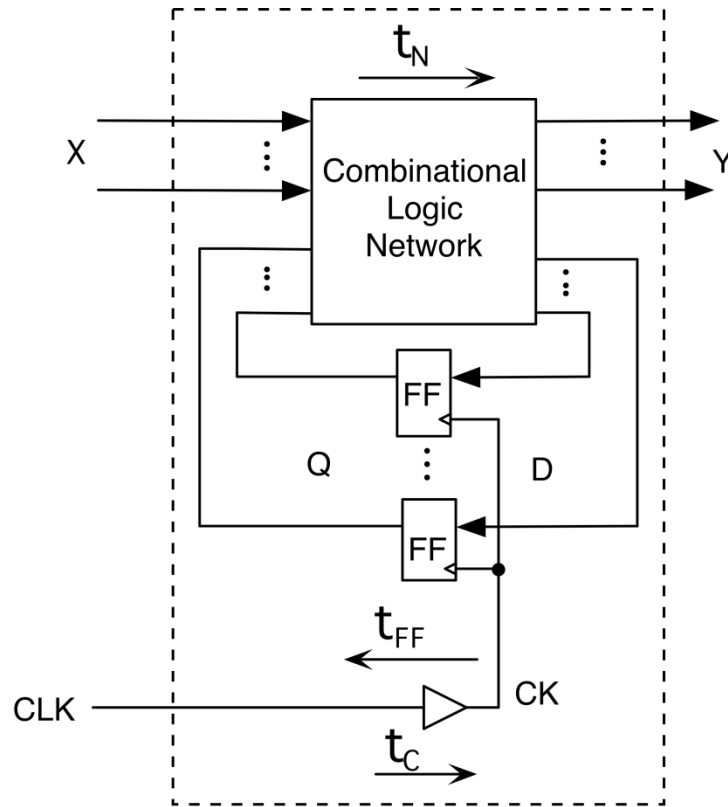


$$T_{SU} = t_{su} + \max t_{PN} - \min t_{PC} \leq t_{su} + \max t_{PN}$$

$$T_H = t_h + \max t_{PC} - \min t_{PN} \leq t_h + \max t_{PC}$$

$$T_P = t_{PFF} + t_{PN} + t_{PC}$$

➤ Example

 


❖ Find T_{SU} and T_H for input signal LD relative to CLK.

$$\begin{aligned}
 T_{SU} &= t_{su} + \max t_{NET} - \min t_C \\
 &= t_{su} + \max t_{INV} + \max t_{NAND} + \max t_{NAND} - \min t_{INV}
 \end{aligned}$$


$$\begin{aligned}
 T_H &= t_h - \min t_{NET} + \max t_C \\
 &= t_h - \min t_{NAND} - \min t_{NAND} + \max T_{INV}
 \end{aligned}$$

Register load control (gating the clock)

 - A very bad way to add a load control signal LD to a register that does not have one is shown below




 - The reason this is such a bad idea is illustrated by the following timing diagram.




- The flip-flop sees two rising edges and will trigger twice. The only one we want is the second one.

 - If LD was constrained to only change when the clock was low, then the only problem would be the clock skew.




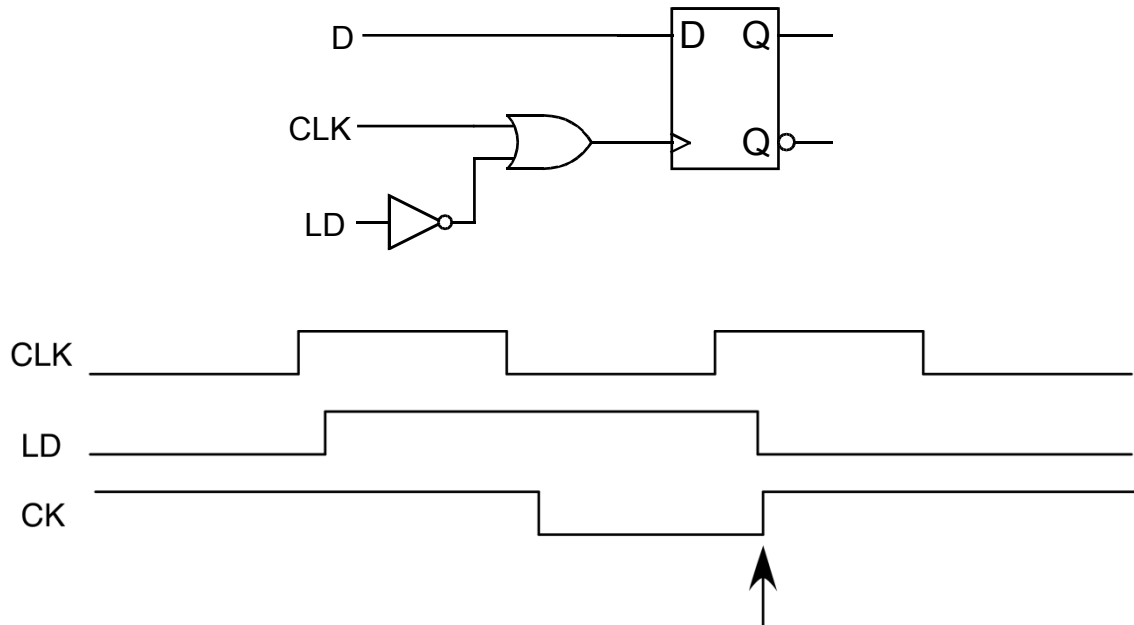- If gating the clock is the only way to control the loading of registers, then use the following approach:



- There is still clock skew, but at least we only have one triggering edge.

 - The best way to add a LD control signal is as follows:




Tips & Tricks

- Use timing diagrams to determine the timing properties of sequential circuits
- Using typical timing values from the data sheet (use only max and/or min values)
- Gating the clock

Detecting timing violations – CASE 1

 (a) Hold time for clocks is 1.5 ns


Determine if there are any timing violations in this design



Detecting timing violations – CASE 2

 
- (a) Hold time for clocks is 1.5 ns
- (b) Clock skew of 3.72 ns between clk20mref and clk10mhz

Determine if there are any timing violations in this design



Detecting timing violations – CASE 3

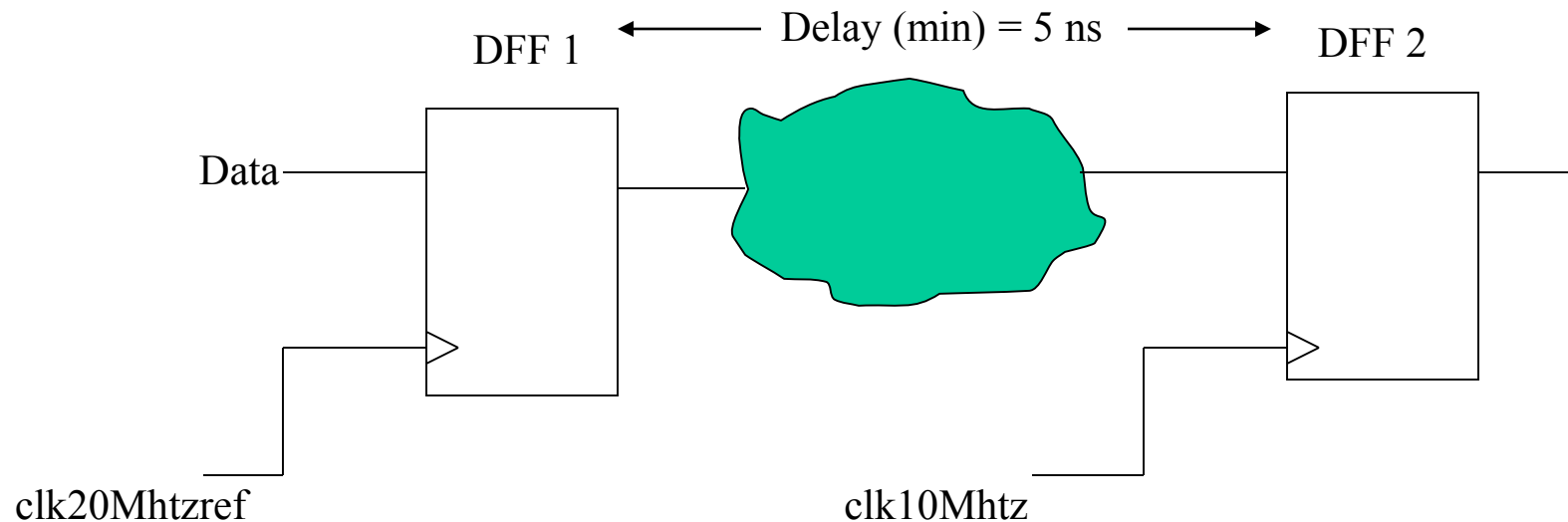
- (a) Hold time for clocks is 1.5 ns
- (b) Clock skew of 3.72 ns between clk20mref and clk10mz



Detecting timing violations – CASE 4

Consider

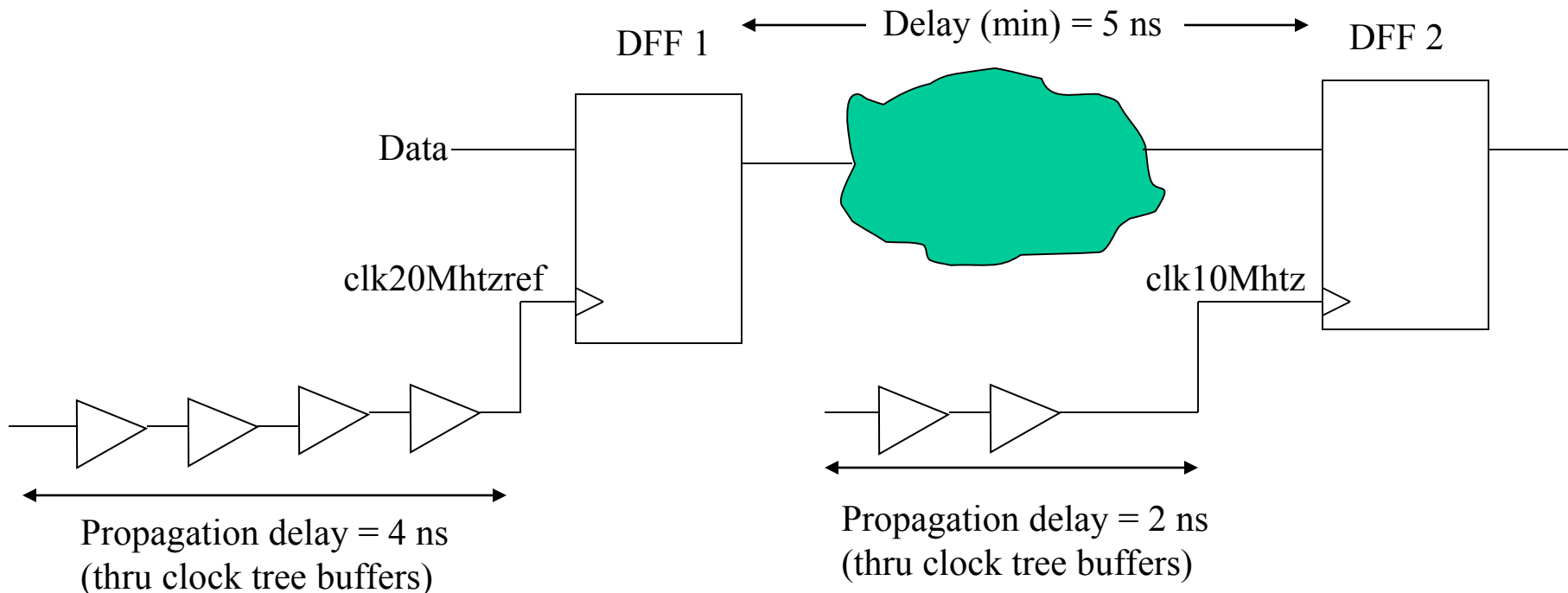- (a) Clock skew of 3.72 ns between clk20mref and clk10mz
- (b) Clock network delays



Thank you