

HDL Design using Verilog


Udit Kumar, PhD, IIT Delhi.

17+ years experience, Author

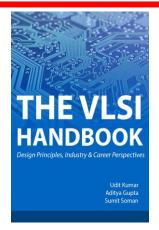https://www.linkedin.com/in/udit-kumar-phd-iit-delhi



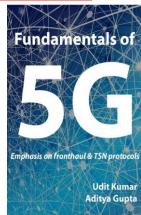

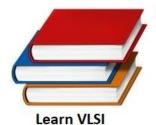

Website: https://www.sites.google.com/view/learnvlsi

LinkedIn: https://www.linkedin.com/company/learnvlsi

Note: Views expressed here are personal views and not endorsed by present or past employer.

Disclaimer



- The intention of this presentation is information sharing. So consider this material as information purpose only.
- We explicitly disclaim any liability for mistakes and omissions in the material presented.
- We have done our best to ensure the correctness of the material and have no obligation or duty to any person or organization for any loss or damages stemming from the contents.
- We make no claim, promises, or guarantees regarding the correctness, completeness, patent infringement, copyright violation or sufficiency of the same.
- Some of materials were copied from the sources freely available on the internet. When possible, these sources have been cited; however, some references may have been cited incorrectly or overlooked. If you feel that a picture, graph, or code example has been copied from you and either needs to be cited or removed, please feel free to email: elearn.vlsi@gmail.com and we will address this as soon as possible.
- Take prior approval for Commercial usage of this information.
- Views expressed here are personal views and not endorsed by present or past employer.

Outline



- Need for HDL Language?
- History
- Where to start: VHDL, Verilog, System Verilog?
- First Step for HDL
- Verilog fundamentals
 - Get familiarize with keywords, syntax, operators, features etc.
 - Testbench
 - Blocking, non blocking, Operators, Flow controls etc.
 - Timescales, inter n intra assignment delay
- Delta Delay
- Steps for RTL Design
- Simulations tools
- Learning resources

Need for HDL Language




- HDL offers a way to model piece of hardware using a text based programming language.
- Synthesis tools convert HDL into logic gates.
- HDL languages
 - Verilog
 - System Verilog
 - VHDL
- Difference from Software
 - Need hardware mindset
 - Work in parallel not sequential like software

History



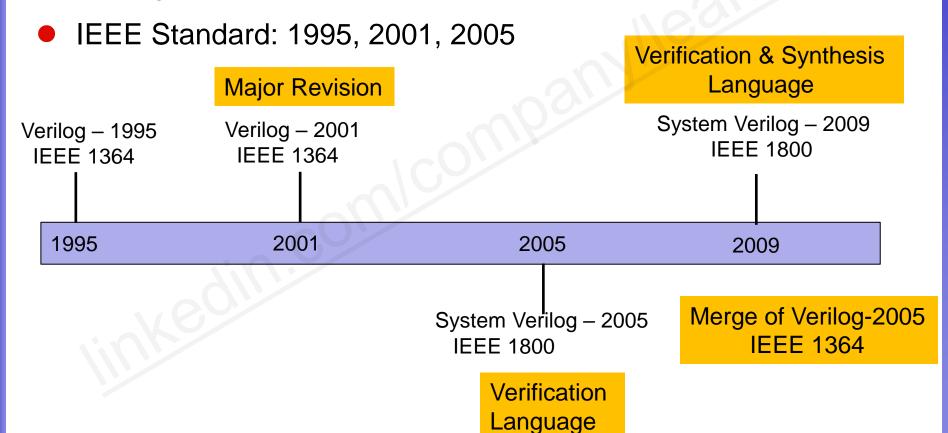
- Developed by Gateway Design Automation (Proprietary Language): 1984
- Verilog made an open Standard: 1990



Verilog and System Verilog




System Verilog is superset of Verilog.

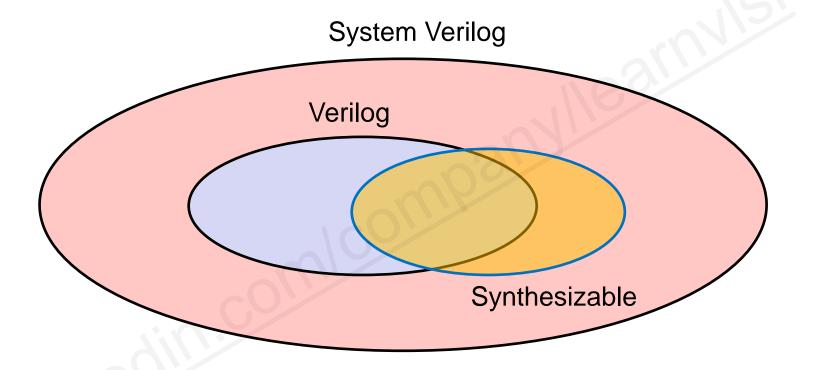

 Both Verilog and System Verilog contains Synthesizable and non synthesizable constructs.


Confusion: Where to start?



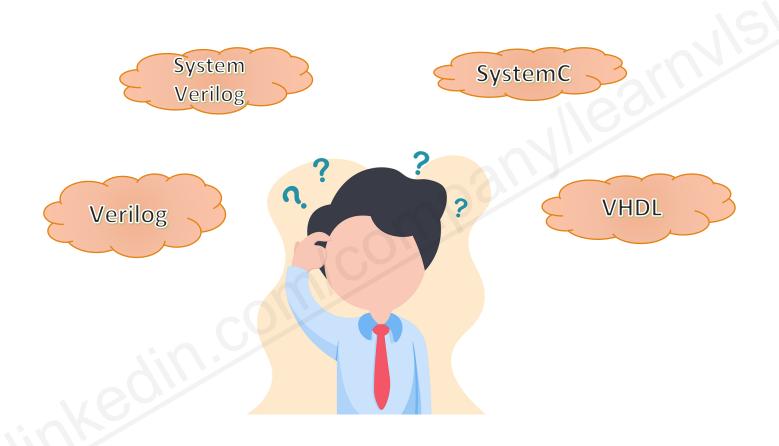

ASIC/IC Language



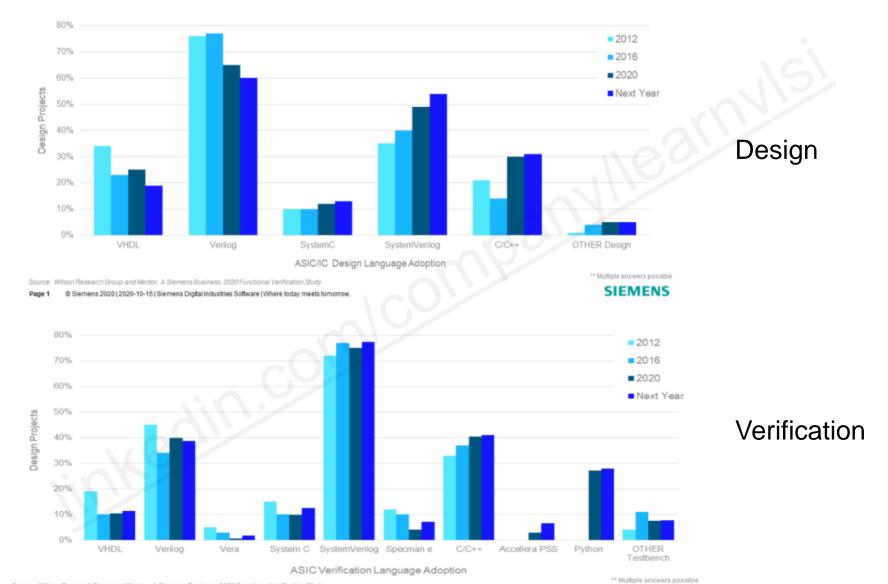


Source: Wilson Research Group and Mentor, A Siemens Business, 2020 Functional Verification Study


SIEMENS

FPGA Design and Verification



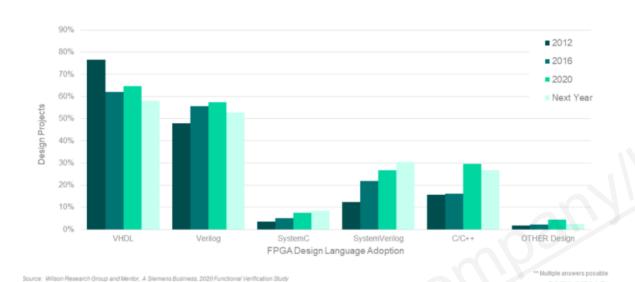

Design

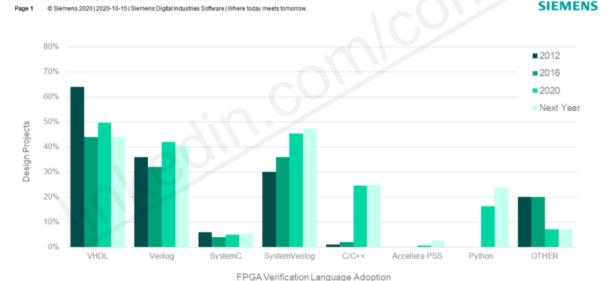


Verification

** Multiple answers possible
SIEMENS

Hard Digital IP Design Flow



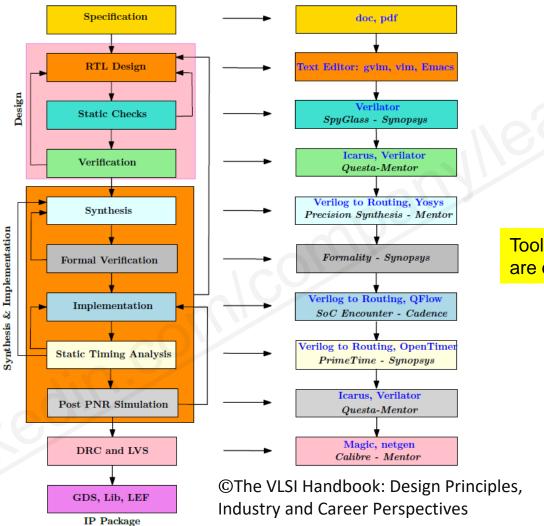


Tools written in blue color are open source tools

Reference: Book "The VLSI Handbook: Design Principles, Industry and Career Perspectives", Udit Kumar, Aditya Gupta, Sumit Soman

First Step for HDL: Hardware Mindset




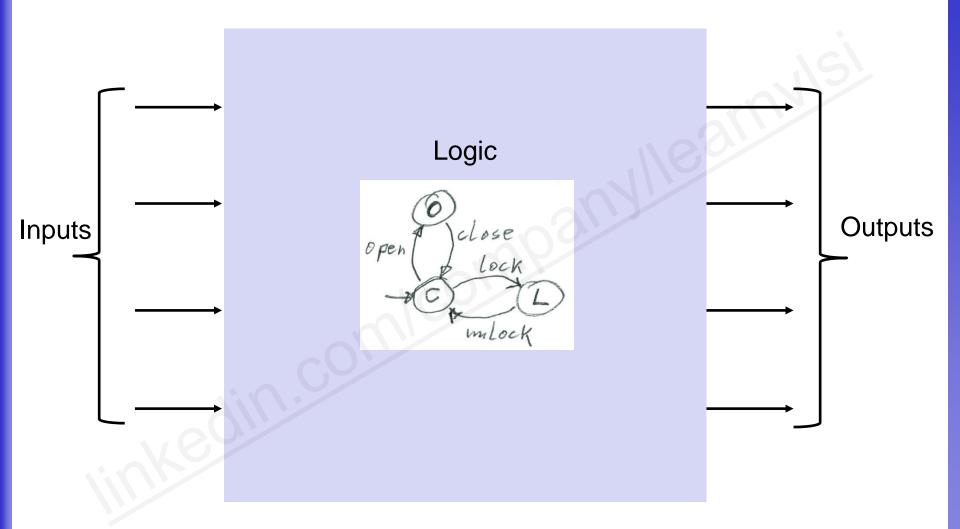


Thinking in terms of digital design is key.

An Example



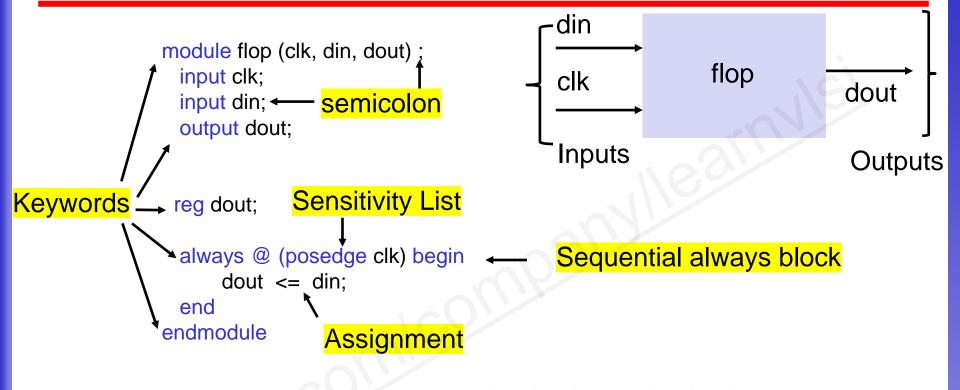

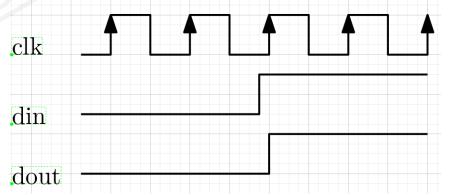

Synchronous and Asynchronous Reset



```
module flop (clk, rst_n, din, dout) ;
module flop (clk, rst_n, din, dout);
                                                            input clk;
 input clk;
                                                            input rst_n;
 input rst_n;
                                                            input din;
 input din;
                                                            output dout;
 output dout;
                                 Difference in the sensitivity list
                                                            reg dout;
 reg dout;
                                                            always @ (posedge clk) begin
 always @ (posedge clk or negedge rst_n) begin
                                                                if (!rst_n) begin
     if (!rst_n) begin
                                    Reset Check
                                                                   dout \le 1'b0;
        dout <= 1'b0; ▼
                                                                end else begin
     end else begin
                               Conditional statement
                                                                   dout <= din:
        dout <= din;
                                                                end
     end
                                                            end
 end
                                                           endmodule
endmodule
             clk
             rst_n
                                                   Sync
                                                              rst_n
Async
             din
                                                   Reset
Reset
                                                              \dim
             dout
                                                              dout
```

Behavioral Vs structural

end else begin


end

end

endmodule

dout <= din;



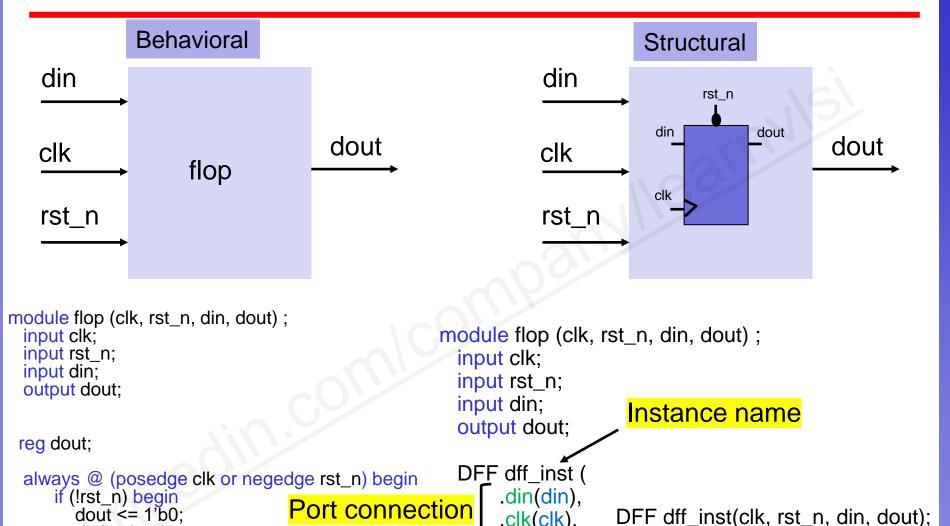

by name

endmodule

.clk(clk),

.rst_n(rst_n),

Port connection

by ordered list

_.dout(dout));


Behavioral Vs Structural



- Behavioral
 - Program describes input/output behavior of circuit
 - Many behavioral implementations could have same behavior.
 - Easier to write and understand



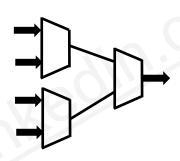- Explicit structure of the circuit
- Useful to build bigger designs.





Behavioral modelling is mostly used to describe functionality. Structural modelling is used to connect various blocks.

Continuous and Procedural Statement



Continuous Assignment

```
module flop (D0, D1, DOUT);
input D0, D1;
output DOUT;
assign DOUT = D0 & D1;
```

Operators

endmodule

module flop (D0, D1, DOI

endmodule

```
module flop (D0, D1, DOUT);
input D0, D1;
output DOUT;

always (D0 or D1) begin
DOUT = D0 & D1;
end;
```

Procedural Assignment

Blocking assignment

- Continuous Statement (assign)
 - Always evaluated,
 - All statement evaluates in parallel
- Procedural Statement (always, initial)
 - Execute in the defined order
 - Two types
 - o always: Executed continuously based upon sensitivity list
 - o initial: Execute only once

Parameter

end

end

endmodule



Default value

```
module flop #(parameter WIDTH=8) (clk, rst_n, din, dout);
input clk, rst_n;
input [WIDTH -1 : 0] din;
output [WIDTH -1 : 0] dout;

reg [WIDTH -1 : 0] dout;

always @ (posedge clk or negedge rst_n) begin
if (!rst_n) begin
dout <= {WIDTH{1'b0}};
end else begin
dout <= din;
```

Let's summarize



```
module <module_name> #(<parameters>) (<port list>);
```

- <Declarations>
- <Continuous statements>
- <Behavioral code>
- <Instantiations>
- <Task and functions>

endmodule

Testbench



Testbench

```
module testbench ();
   reg clk = 1'b0;
   reg rst_n;
   reg din;
   wire dout;
initial begin
 forever
   #10 clk = ! clk;
end
initial begin
 din = 1'b0;
 rst_n = 1'b0;
 #25 rst_n = 1'b1;
 # 7 din
           = 1'b1;
end
flop F1 (clk, rst_n, din, dout);
endmodule
```



DUT

```
module flop (clk, rst_n, din, dout);
input clk;
input rst_n;
input din;
output dout;

reg dout;

always @ (posedge clk or negedge rst_n) begin
    if (!rst_n) begin
        dout <= 1'b0;
    end else begin
        dout <= din;
    end
end
end
endmodule</pre>
```

Can we use always Vs initial forever for clock generation?



- Yes, both approach are fine
- Approach 1 reg clk = 1'b0;

```
Always
#10 clk = ! clk;
end

always @ (*)
#10 clk = ! clk;
end

Always @ (clk)
#10 clk = ! clk;
end

always @ (clk)
clk = ! clk;
end
```

Approach 2
 reg clk = 1'b0;
 initial begin
 forever
 #10 clk = ! clk;
 end

Scaler, Vectors and Arrays



wire busA; // Single bit scaler net
wire [3:0] busA // 4-bit vector net



3 2 1 0

wire [3:0] busA [2]

3	2	1	0
3	2	1	0

Numbers representation



```
Format

Value

Size 

4'b1010 // 4-bit binary number for 10

4'hB // 4- bit hex number

4'd10 // 4-bit decimal number
```

Operators



- Arithmetic Operators
 - +, , ..*
- Bitwise Operators
 - &, |, ^ ..: Work on each bits (A=3'b101 B= 3'b100, Q = A &B = 3'b100)
- Reduction Operators
 - &, |, ^, ~...: Reduces a vector to a single bit value (&A = 'b0)
- Relational Operators
 - **⊙** >, <, >= ...
- Logical Operators
 - !, &&, || ...
- Shift Operators
 - <<, >>, <<<, >>> (A=8'b010, B = A << 2 = 8'b01000)
 </p>
- Equality Operators

Find out issue in the code?



```
module flop (clk, rst_n, din, dout);
module flop #(parameter WIDTH=8) (clk, rst_n, din, dout);
                                                                  parameter WIDTH=8;
 input clk, rst_n;
                                                                  input clk, rst_n;
 input [WIDTH -1:0] din;
                                                                  input [WIDTH -1:0] din;
 output dout;
                                                                  output dout;
reg dout;
                                                                 reg dout;
 always @ (posedge clk or negedge rst_n) begin
                                                                  always @ (posedge clk or negedge rst_n) begin
     if (!rst_n) begin
                                                                      if (!rst_n) begin
        dout \le \{WIDTH\{1'b0\}\};
                                                                        dout \le \{WIDTH\{1'b0\}\};
     end else begin
                                                                      end else begin
        dout <= din;
                                                                        dout <= din;
     end
                                                                      end
 end
                                                                  end
endmodule
                                                                endmodule
```

Flow controls



- Control statement
 - If, for, while
 - case, casex, casez
 - ...
- Initial/forever: What will be output for these code?

```
module forever_example (clk_out);
output clk_out;

reg clk_out = 1'b0;

initial begin
    #10 clk_out = ! Clk_out;
end
endmodule

module forever_example (clk_out);
output clk_out;

reg clk_out = 1'b0;


initial begin
forever
#10 clk_out = ! Clk_out;
end
endmodule
```

Blocking vs non-blocking assignments



Delta delay occurrence in such assignments

Start of delta time

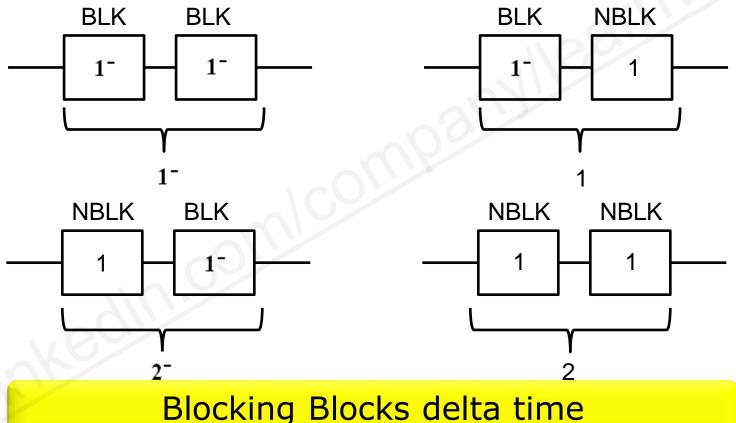

BLK: Blocking assignment, **NBLK:** Non-Blocking assignment

An example



```
// Blocking assignment
always @ (A or B)
begin
S1 = (A || B);
end
```

```
always @ (posedge clk)
begin
Q = S1;
end
```

-- No delta cycle consumed

// Non blocking assignment

always @ (posedge clk) begin S3 <= S2; Q <= S3; end

-- 1 delta cycle consumed

Verilog timescale



- Verilog uses time delays defined in units.
- Mapping time units to "real" time is done using `timescale
- `timescale <time_unit> / <time_precision>
 - Time_unit: this is the time unit \(\psi\) sed to defined delays
 - Time_precision: Minimum time incremented by simulator
 - Example
 `timescale 1ns/1ps
 initial begin
 q = 1'b0;
 #5 q = 1'b1; // ← 5 ns delay will be observed end

Fork/Join




```
initial begin


#5 c = 1;


#5 b = 0;

#5 d = c;
end

Execute sequentially
```

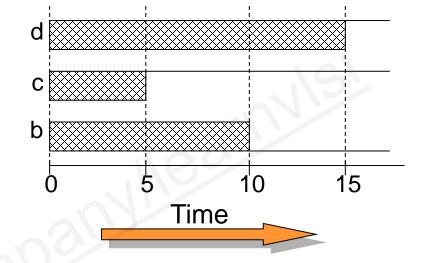

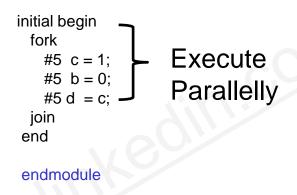

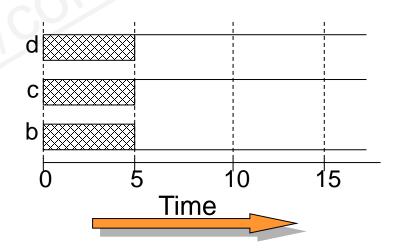

Intra and Inter assignment delay



Intra assignment delay

```
<LHS> = #<delay> <RHS>
  module flop (clk, rst n, din, dout);
    input clk;
    input din;
    output dout;
   reg dout;
    always @ (posedge clk) begin
        dout <=#1 din:
    end
  endmodule
```

Considered as transport delay

Inter assignment delay

```
#<delay> <LHS> = <RHS>
module forever_example (clk_out);
output clk_out;


reg clk_out = 1'b0;
initial begin
  #10 clk_out = ! Clk_out;
end
endmodule
```

Wait for elapse of the time and than evaluate the expression

What is Delta Delay?



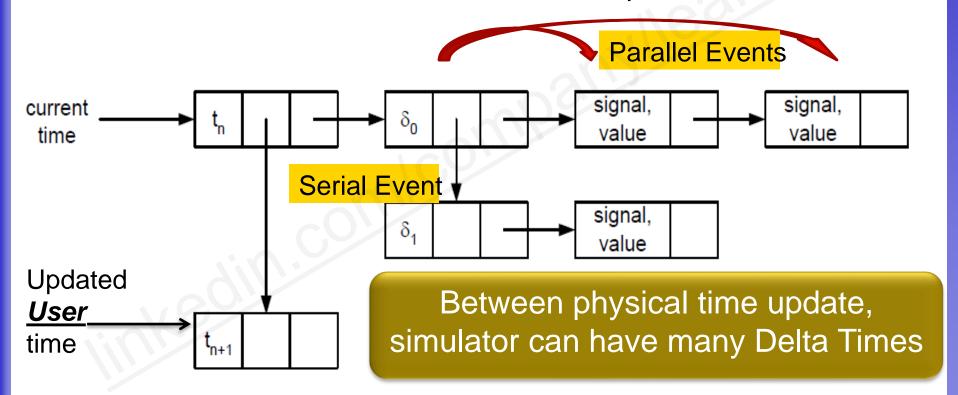- A delta time, used <u>inside</u> simulator database, is infinitely small but useful...
- Each event consumes one delta time-step.



Verilog has event queue



always @ (A or B)

S1 = (A || B); $S2 \le A \&\& B;$

begin

end

Active event

- Blocking assignments
- Continuous assignment
- Evaluate RHS of non-blocking assignment

Inactive events

#0 blocking assignments

Non-blocking

Update LHS of non-blocking assignments


Monitor events

\$monitor & \$strobe

Multiple events are grouped together and execute in defined order.

Concept of Parallel & Serial events



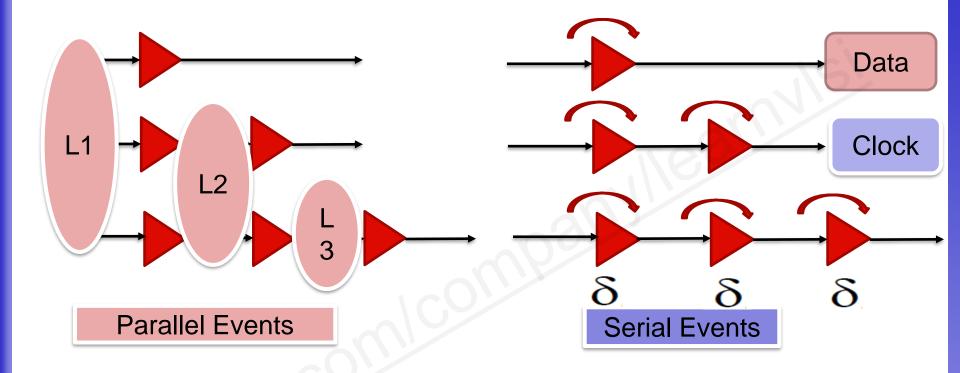


- All events are software objects & consume "Delta" delay.
- Simulators do not understand relationship between data & clock events.

Discrete Event Simulation



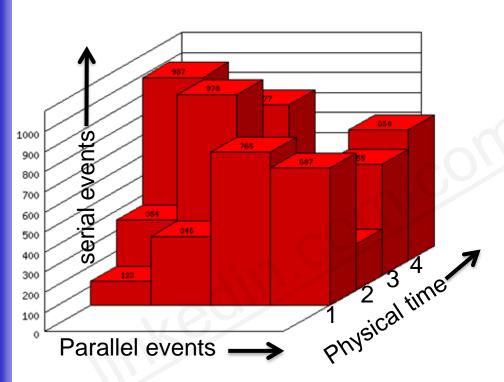 A method to mimic events in physical systems, <u>using</u> software.




- Language Rules (LRM) specifies how and when events are created and updated.
- Simulator manages millions of events and their order (explained later)
- Understanding this is useful to debug corner cases.

HDL writing affects events



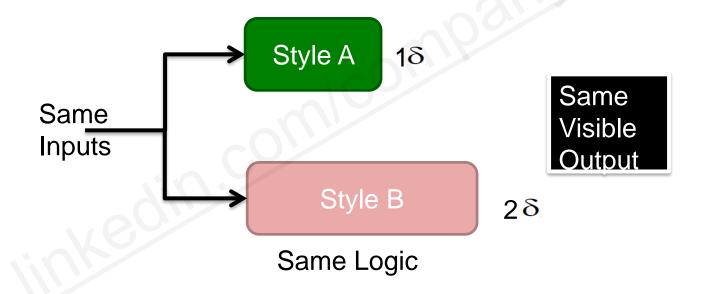
- HDL writing affects creation and flow of events.
- The result visible to user is the same, ir-respective of HDL style. As simulator do not show simulated result for each delta to the users.




Style A: Output coming after 1 Delta




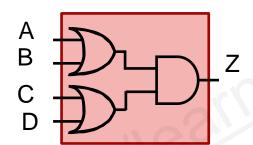
always @ (A or B or C or D) begin $Z \leftarrow (A \parallel B) \&\& (C \parallel D)$; end



Test case

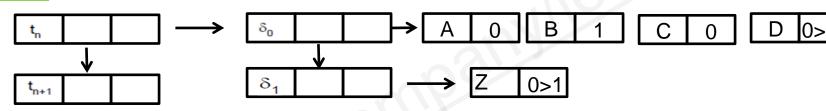


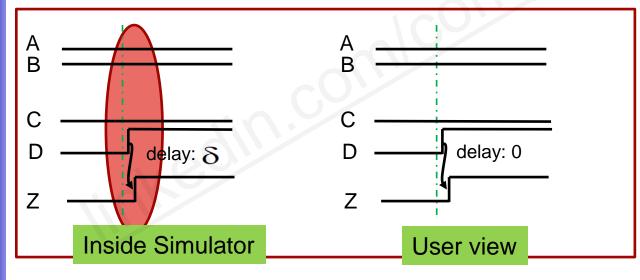

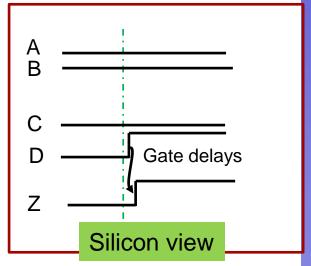


Style B: Output coming after 2 Delta



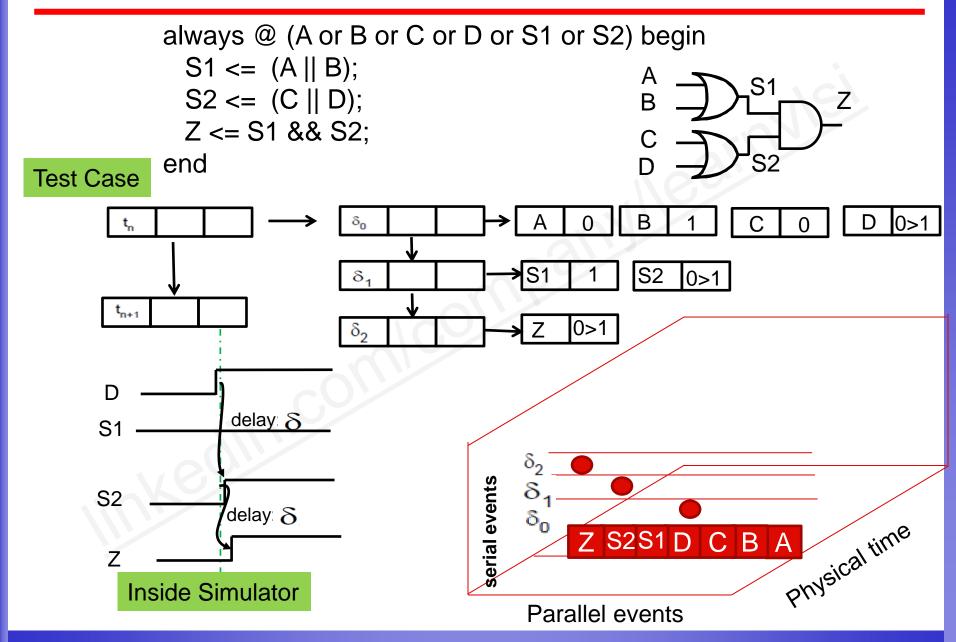

Style B with Multiple Input Changes




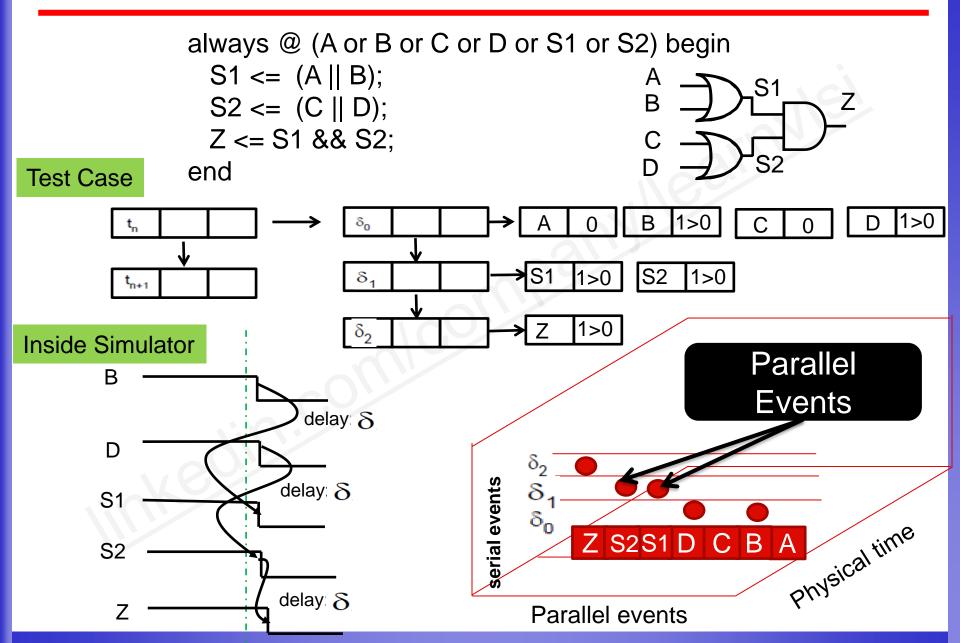



Style B: RTL & Silicon view



Always @ (A or B or C or D) begin S1 <= (A || B); S2 <= (C || D); O <= S1 && S2; end

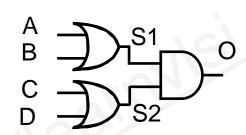

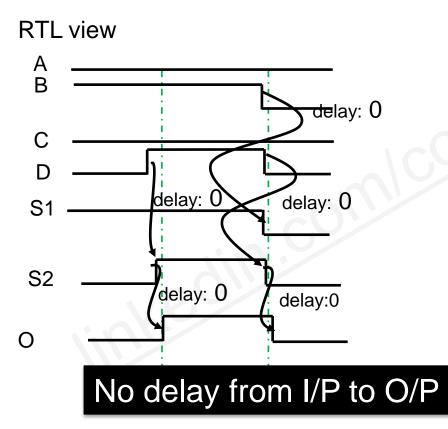


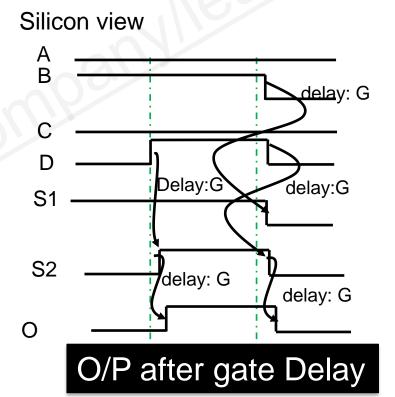

Delta delay and Physical delay



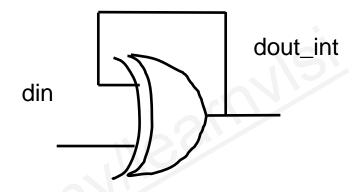
```
reg dout_int=0;
always @ (din or dout_int) begin
  dout_int <= dout_int ^ din;
end</pre>
```



RTL Simulation will hang



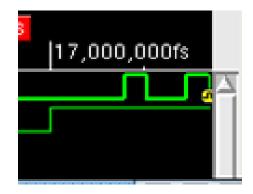 Gate level simulation will produce train of pulse



RTL Simulation hangs but gate level simulation produces train of pulses.

Design examples




- Clock gating
- Clock dividers
- Up counter
- Level to pulse generator
- Pulse to level generator
- Sequence detector
- FSM designs

Steps for RTL Design



- Draw a block diagram and mention input and outputs.
- Decide on the clock and reset
- Do you need to break functionality in multiple blocks? If yes, draw sub block level diagrams.
- Does your design require some sequence of operation? If yes, map desired functionality into a FSM.
- Think in terms of what state you want to store on every clock cycle.
 - This will help you to find out required flops, that you are going to put into the sequential always block.

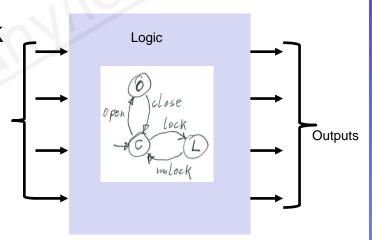

UP Counter




```
din
                                            clk
module flop #(parameter WIDTH=4)
                                                                    count
     (input clk, rst_n, en, output [WIDTH-1:0] count)
                                             en
                                                                     Outputs
reg [WIDTH-1:0] counter;
                                             Sequential always block
 always @ (posedge clk or negedge rst_n) begin
    if (!rst_n) begin
      count <= 1'b0;
    end else begin
                             Combinational logic
      if (en) begin
       count <= count + 1;
      end
    end
               Flops
 end
endmodule
               count
    clk
```

Synchronous FIFO Design



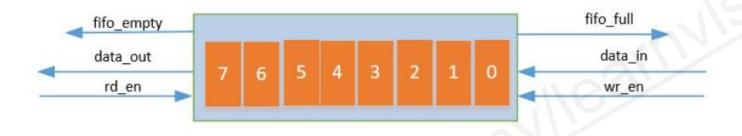Assignment: Lets design a Synchronous FIFO with depth 32, and width 8.



Write Control

RAM

Read Control

FIFO full and FIFO Empty

Simulation tools



- Open Source tools
 - Icarus Verilog: <u>www.iverilog.icarus.com</u>
 - Verilator: <u>www.veripool.org/wiki/verilator</u>
- Commercial tools
 - Cadence: ncsim
 - Mentor: Questa
 - Synopsys: vcs
- Web based simulator
 - https://www.edaplayground.com/
- Useful utilities: https://edautils.com/DownloadLinks.html

Learning Resources



- Book: VERILOG HDL, by Samir Palnitkar
- Verilog FAQ by Shivakumar
 - Various FAQ on Verilog
 - Good collection of interview Questions: A must read before Interviews
- https://www.sites.google.com/view/learnvlsi
- https://www.vlsiguru.com/mentor-verilog-hep-ppt/
- https://www.chipverify.com/verilog/

Questions and Answers

- Async reset should be used as active low or high?
 - Usage of active low async reset is higher.
 - Active low async reset is helpful to save power, and better noise immunity, better control to bring whole design into reset state.
- Can we use posedge clock along with posedge of rst_n in sensitivity list?
 - Yes, we can use.
- Can we use "and" in sensitivity list
 - No, this is not allowed.
- Which one is better, Async or sync reset?
 - Async reset is good when we want to control design reset externally and want reset immediately. Majority of design using Async reset.
 - Sync reset is part of data path and generally internally generated signals. This is used on need basis.
 - For area optimization in the data path, there are flops without async or sync reset.

Link for other presentations



- HDL Design using Verilog
 - https://www.linkedin.com/feed/update/urn:li:activity:6901101173491798016
- RTL Design Guidelines
 - https://www.linkedin.com/feed/update/urn:li:activity:6903289386536968192
- Clock domain crossing:
 - https://www.linkedin.com/feed/update/urn:li:activity:6906226196003061760
- Low Power Design:
 - https://www.linkedin.com/feed/update/urn:li:activity:6913837834302885888
- Low Power RTL Design
 - https://www.linkedin.com/feed/update/urn:li:activity:6914792874811297793
- Power optimization at Architecture and implementation level
 - https://www.linkedin.com/feed/update/urn:li:activity:6915873128191590400
- VLSI Design Flows and Open source tools:
 - https://www.linkedin.com/feed/update/urn:li:activity:6886886690405924864

Learn VLSI website: https://www.sites.google.com/view/learnvlsi/webinar



Telegram Channel: https://t.me/elearnvlsi

For more updates, follow Learn VLSI LinkedIn Page: https://www.linkedin.com/company/learnvlsi

Feedback/Errata: Please send email to elearnvlsi@gmail.com


After each improvement, the updated slides will be available at website: https://www.sites.google.com/view/learnvlsi/webinar

ADDITIONAL INFORMATION

What is Shoot-thru?



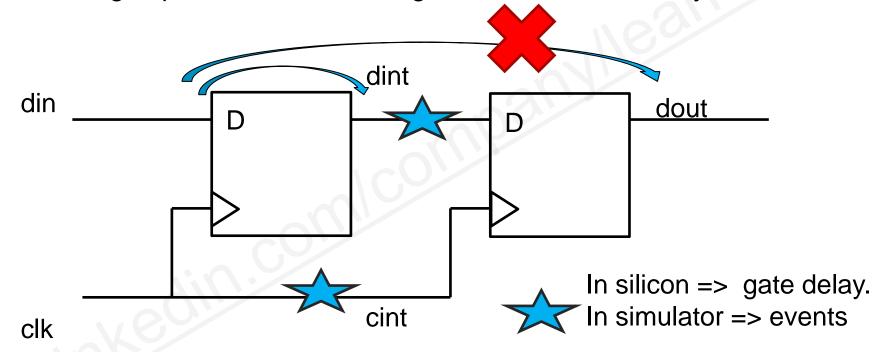- When any signal jumps over an extra register within one clock cycle.
 - E.g. Input "din" crosses 2 register within one clock cycle.




Shoot-thru:

(events in data path) <= (events in clock path)

How Simulation Shoot-thru occurs?



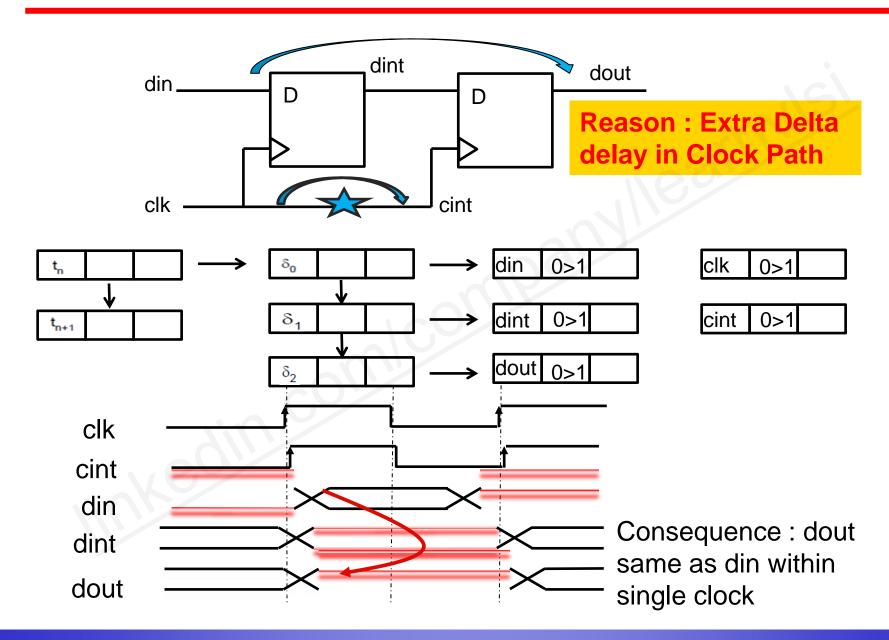


Will Verilog coding rules help?



Can blocking assignment in combination blocks and nonblocking in sequential avoid simulation shoot-thru?

Not, always....

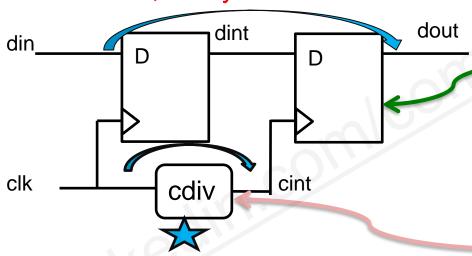

Extra Delta-delay in Clock Path

```
// Input data sampling
```

// Capture data on divided clock

// Clock generation


```
always @ (posedge clk, negedge rst_n) begin if (rst_n==1'b0) cint <= 1'b0; else cint <= !cint:
```

Non-blocking assignments consume delta delay

So, How to detect shoot-thru issues?



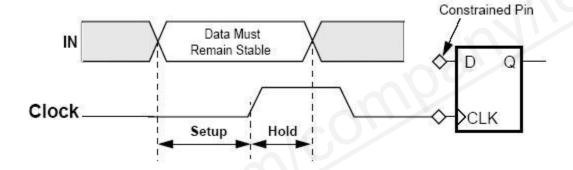- By using an improved simulator?
 - NO, as root cause of problem is that RTL Simulation has no notion of timing delay & Hold checks.




- By doing Gate level simulation?
 - Yes but it is very costly.
- By using robust RTL coding rules?
 - Yes this is easy and efficient (see subsequent slides)

Rule 1 - Force scheduling of data



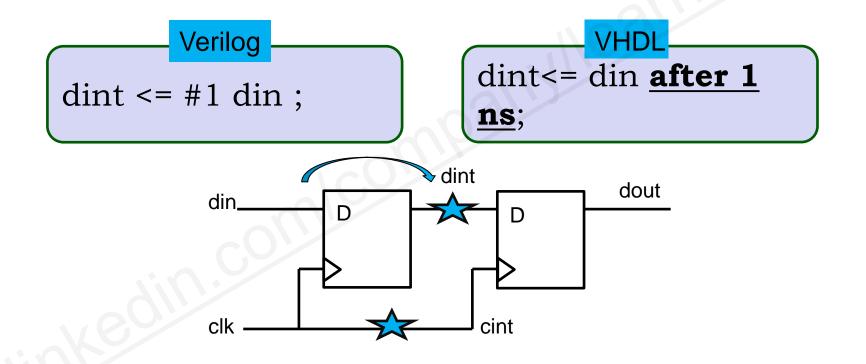
- Force physical time delay in sequential data paths i.e.
 - Sequential data assignment is delayed in 'physical time', instead of 'delta' time.



This ensures there is extra delay in data.

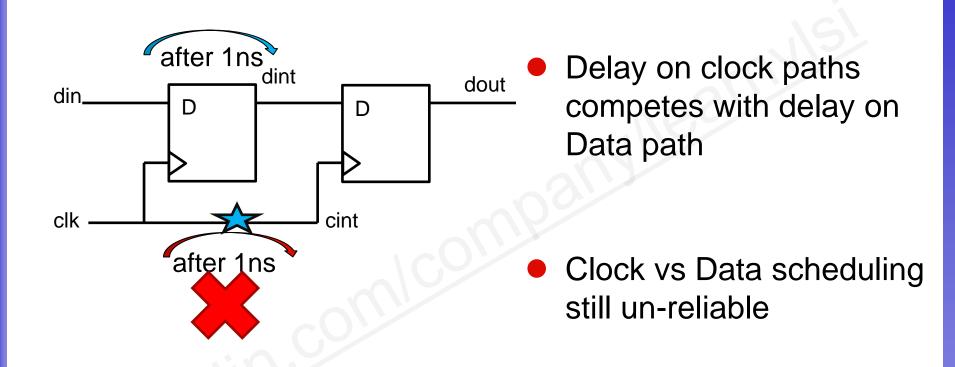Rule 2 - No 'physical delay' in clock path





This ensures a minimum delay on clock path.

Rule1 + Rule2 ensure that data is updated after clock → no risk of shoot-thru